

# **ECEN 615**

## **Methods of Electric Power Systems Analysis**

### **Lecture 3: Per Unit, Ybus, Power Flow**

---

Prof. Tom Overbye  
Dept. of Electrical and Computer Engineering  
Texas A&M University  
[overbye@tamu.edu](mailto:overbye@tamu.edu)



# Announcements

---



- Exam 1 is moved to Oct 13 (Oct 10 and 11 are fall break)
- Homework 1 is assigned today. It is due on Thursday September 8
- ERCOT is having a Virtual College Day on September 16 at 930am (Central Time); details at [ERCOT.COM/CAREERS](http://ERCOT.COM/CAREERS)
  - To register you can go to [www.ercot.com/careers/edp](http://www.ercot.com/careers/edp)

The poster features a collage of images: a control room with multiple monitors displaying data, a map of the Texas power grid, and a group of seven diverse young adults standing in front of a large solar panel array. The text is arranged in a clean, modern layout with a teal and white color scheme.

**ercot**

# REGISTER VIRTUAL COLLEGE DAY

EVENT DATE  
**SEPT. 16, 2022**  
9:30 A.M. CDT

REGISTER BY  
**SEPT. 8, 2022**

SHAPE THE FUTURE OF THE TEXAS ELECTRIC GRID.  
LEARN ABOUT OUR CAREER PROGRAMS AT:  
[ERCOT.COM/CAREERS](https://ercot.com/careers)

LEARN

- ◆ Informational panel of ERCOT engineers
- ◆ Overview of ERCOT operations
- ◆ Individual resume consultations
- ◆ Application details for ERCOT's program



Sign Up

# ERCOT Virtual College Day



To register you can go to  
[www.ercot.com/careers/edp](https://www.ercot.com/careers/edp)

# Brief History of Electric Power

---



- First real practical uses of electricity began with the telegraph (1860's) and then arc lighting in the 1870's
- Early 1880's – Edison introduced Pearl Street dc system in Manhattan supplying 59 customers
- 1884 – Sprague produces practical dc motor
- 1885 – invention of transformer
- Mid 1880's – Westinghouse/Tesla introduce rival ac system
- Late 1880's – Tesla invents ac induction motor
- 1893 – Three-phase transmission line at 2.3 kV

# History, cont'd

---



- 1896 – ac lines deliver electricity from hydro generation at Niagara Falls to Buffalo, 20 miles away; also 30kV line in Germany
- Early 1900's – Private utilities supply all customers in area (city); recognized as a natural monopoly; states step in to begin regulation
- By 1920's – Large interstate holding companies control most electricity systems
- 1935 – Congress passes Public Utility Holding Company Act to establish national regulation, breaking up large interstate utilities (repealed 2005)
  - This gave rise to electric utilities that only operated in one state
- 1935/6 – Rural Electrification Act brought electricity to rural areas
- 1930's – Electric utilities established as vertical monopolies

# History, cont'd

---



- Frequency standardized in the 1930's
- During 1940's to 1960's utilities gradually interconnected their systems so by 1970 transmission lines crisscrossed North America, with voltages up to 765 kV
- 1970's brought inflation, increased fossil-fuel prices, calls for conservation and growing environmental concerns
- Increasing rates replaced decreasing ones
- As a result, U.S. Congress passed Public Utilities Regulatory Policies Act (PURPA) in 1978, which mandated utilities must purchase power from independent generators located in their service territory (modified 2005)
- PURPA introduced some competition


# History, cont'd

---



- Major opening of industry to competition occurred as a result of National Energy Policy Act of 1992
- This act mandated that utilities provide “nondiscriminatory” access to the high voltage transmission
- Goal was to set up true competition in generation
- Result over the last few years has been a dramatic restructuring of electric utility industry (for better or worse!)
- Energy Bill 2005 repealed PUHCA; modified PURPA
- Electric grid restructuring took place in the 1990’s into the 2000’s
  - Goal has been to reduce rates through the introduction of competition and consumer choice
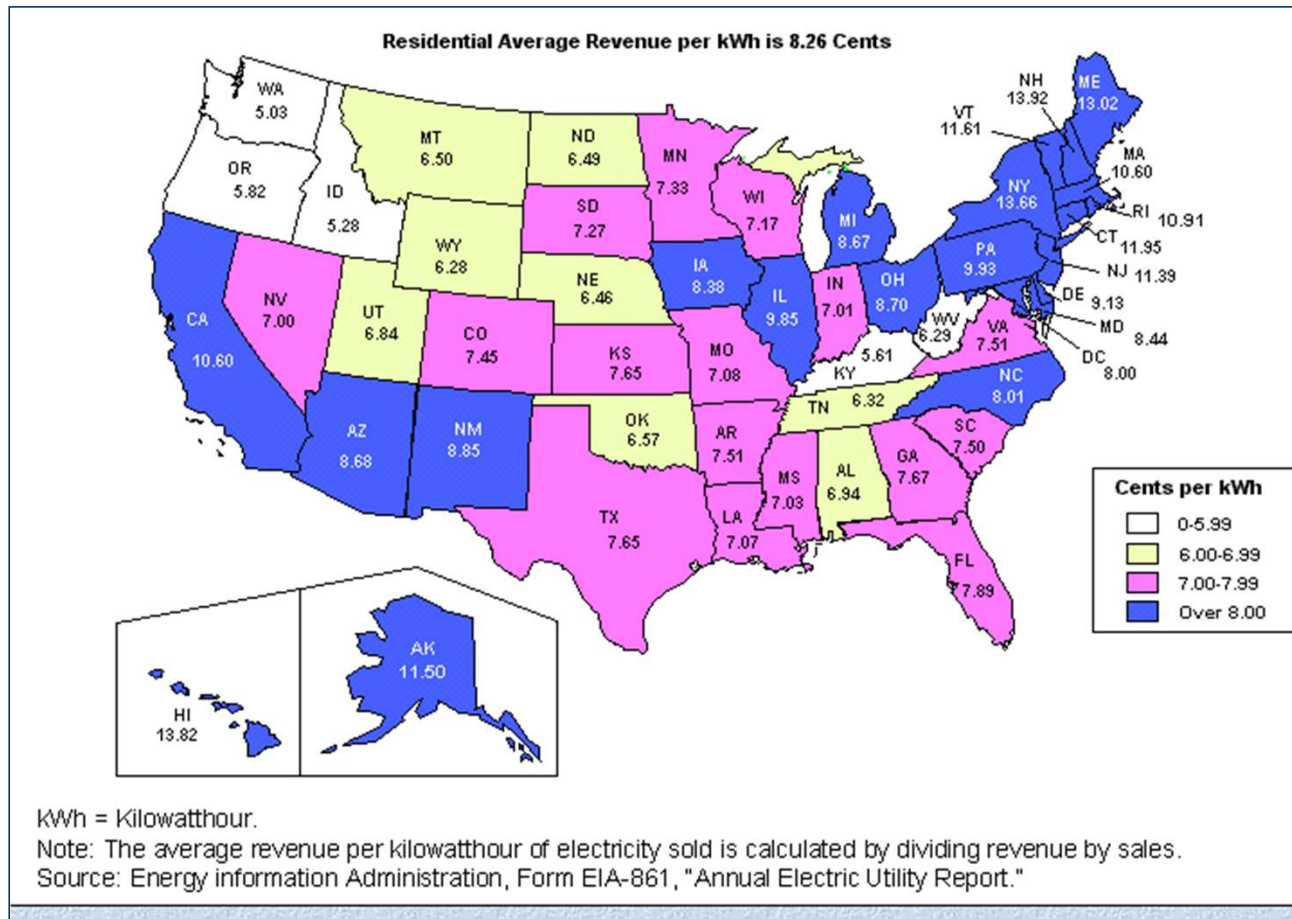
# Historical State Variation in Electric Rates







# August 14<sup>th</sup>, 2003 Blackout
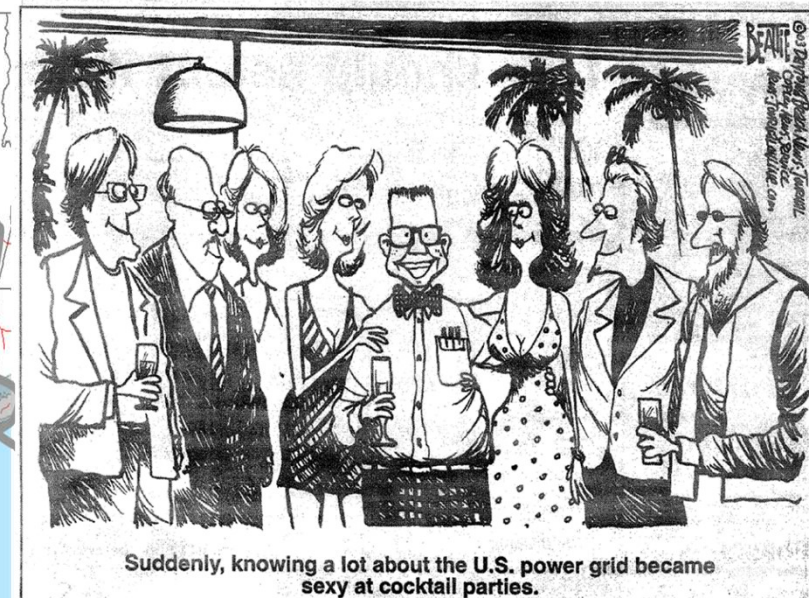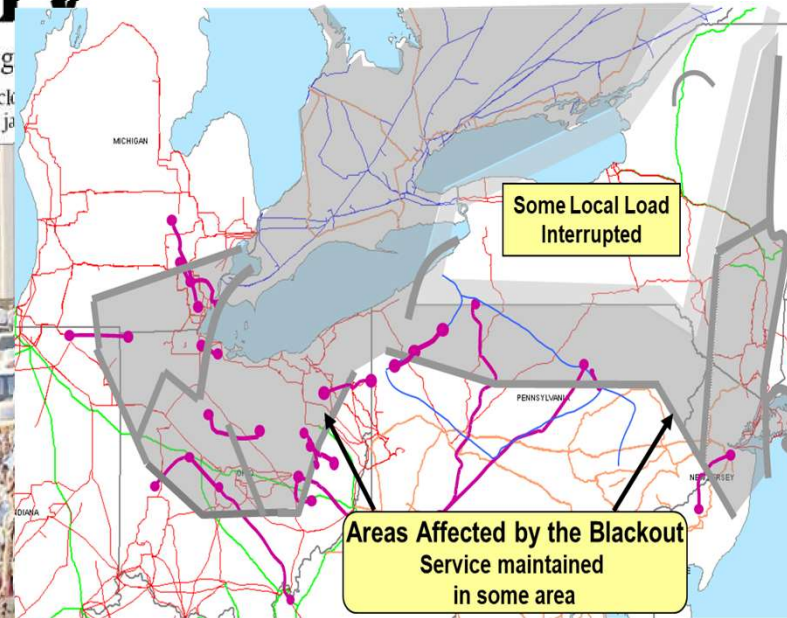
## Blackout misery

50 million affected in Northeast and beyond as power grid


Transportation Many 'wait it out,' by air and land 4A Scenes Moms in labor, cars stuck in car washes 5A Impact Offices closed, cellphones jammed



Above image from energy.gov, August 14, 2003  
Blackout Final Report


I will talk about this event and the 2021 Texas one later in the semester
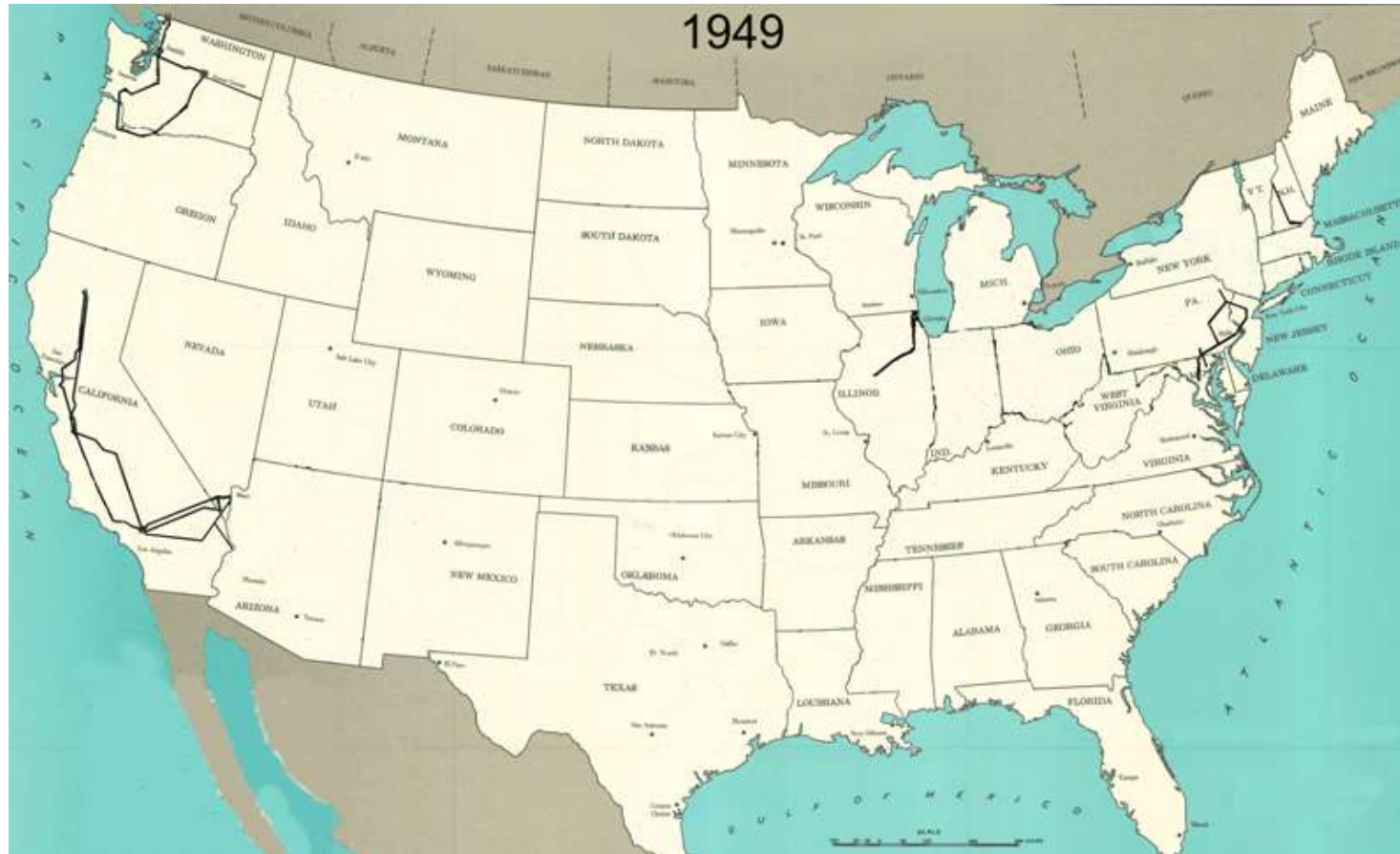
# 345 kV+ Transmission Growth at a Glance (From Jay Caspary)






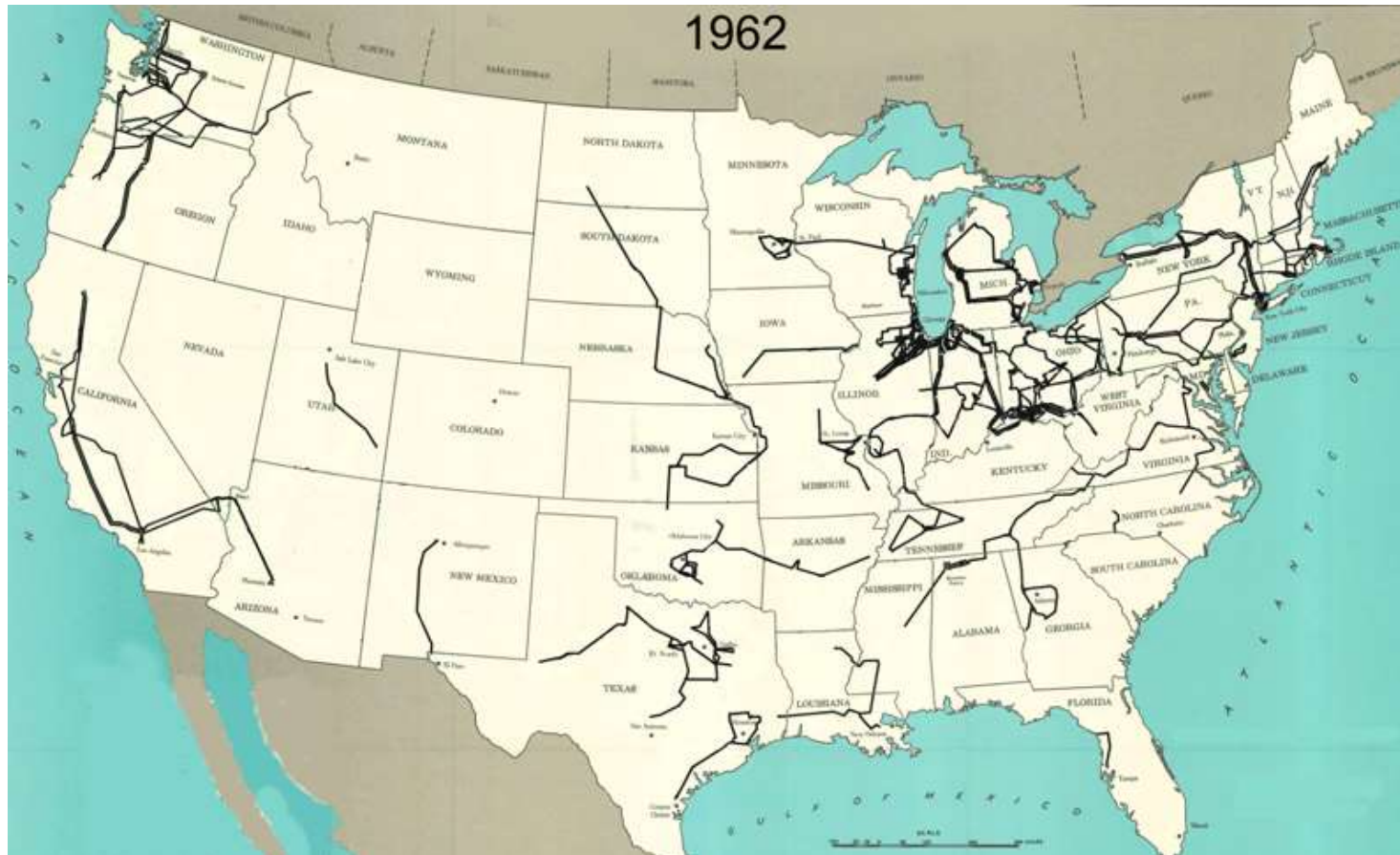
# 345 kV+ Transmission Growth at a Glance (From Jay Caspary)


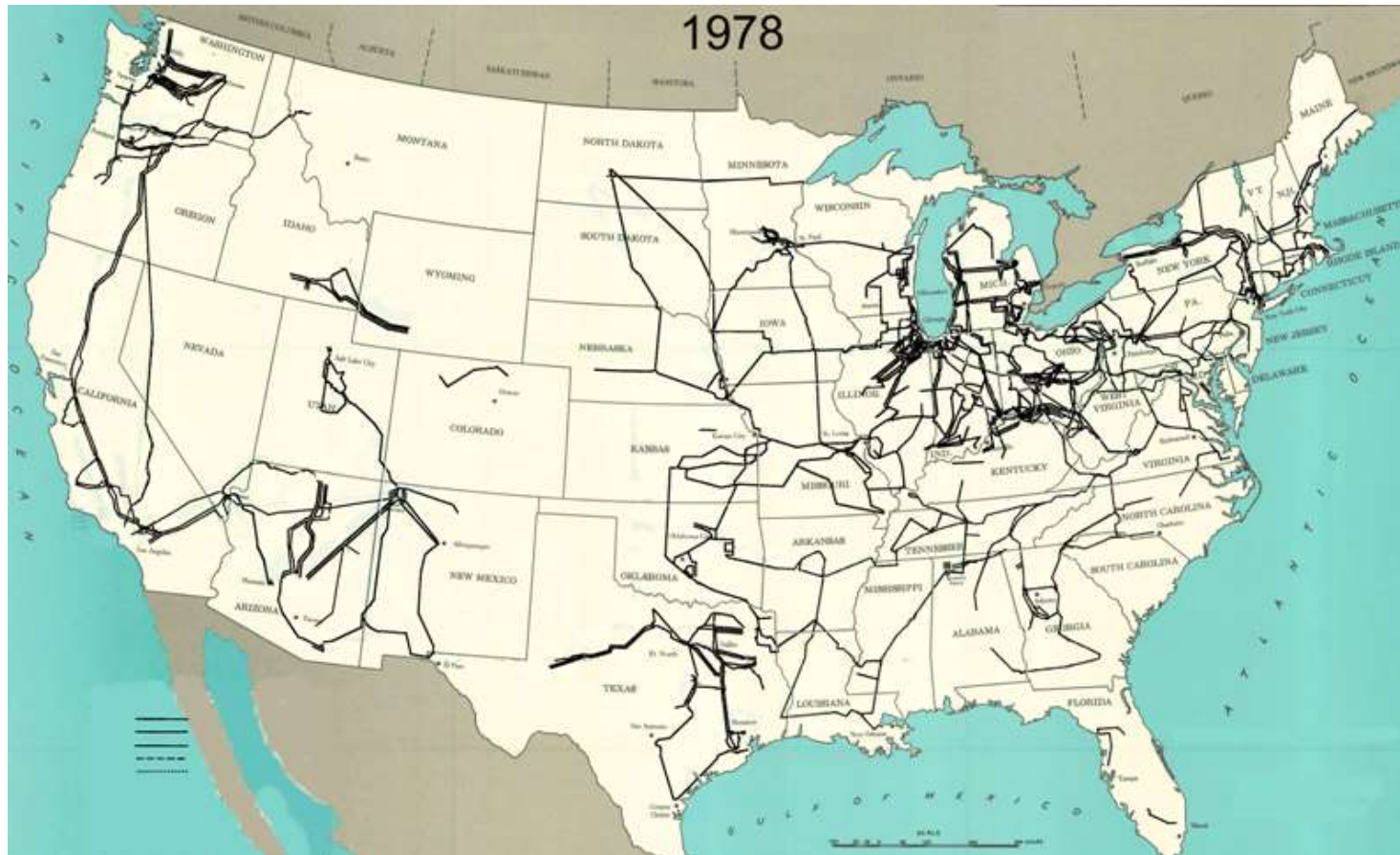
# 345 kV+ Transmission Growth at a Glance (From Jay Caspary)


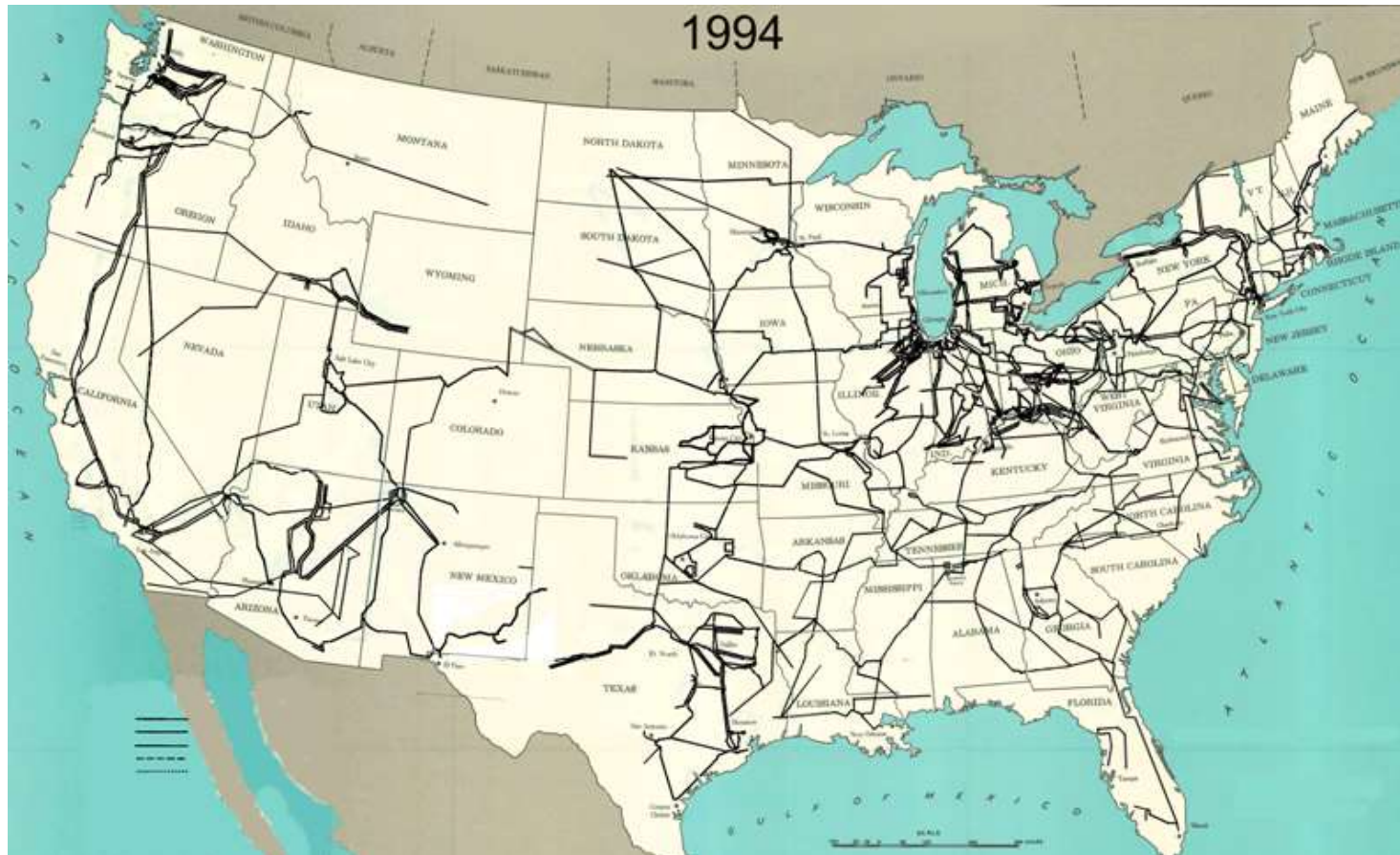
# 345 kV+ Transmission Growth at a Glance (From Jay Caspary)






# The Smart Grid



- The term “Smart Grid” dates officially to the 2007 “Energy Independence and Security Act”, Title 13 (“Smart Grid”)
  - Use of digital information and control techniques
  - Dynamic grid optimization with cyber-security
  - Deployment of distributed resources including
  - Customer participation and smart appliances
  - Integration of storage including PHEVs
  - Development of interoperability standards


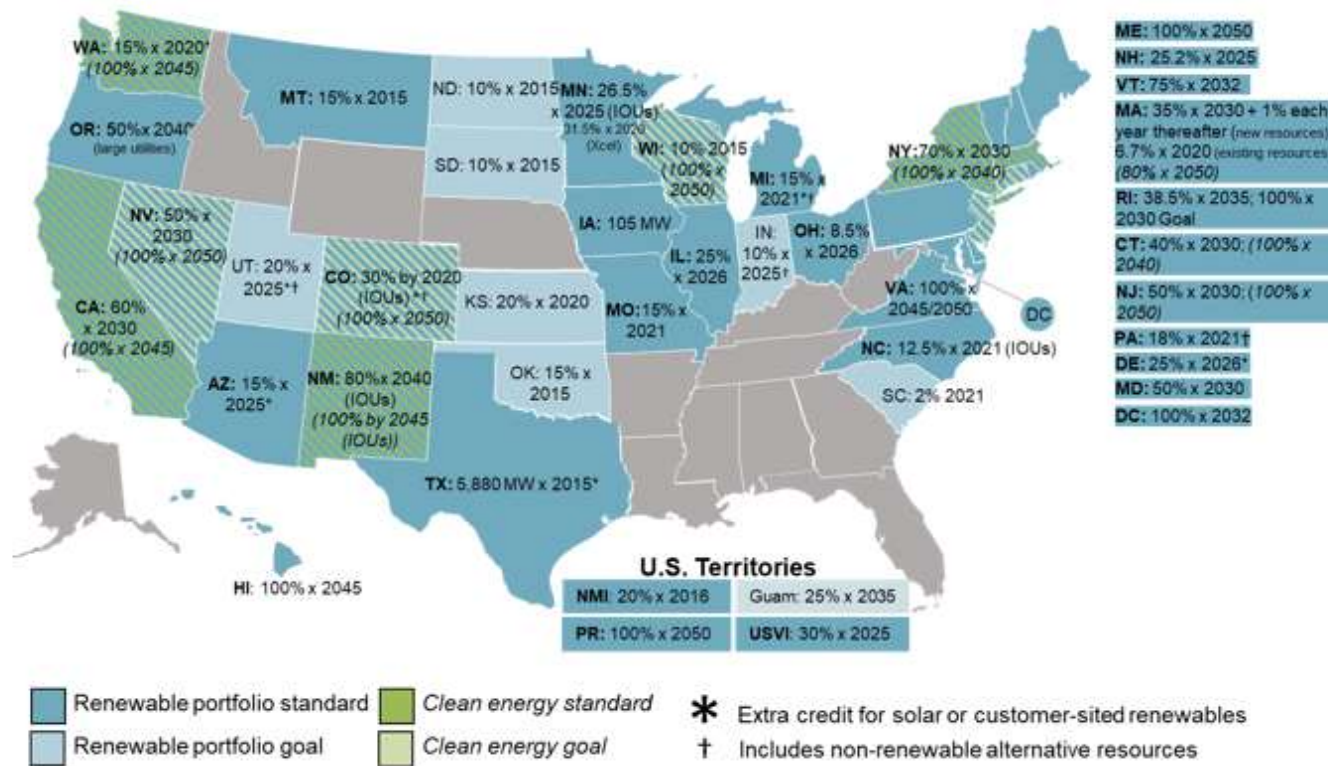
# Renewable Portfolio Standards (September 2020)



TX is now 10 GW by 2025 which we've met several times over; CA is 60% by 2030 and 100% by 2045

Image source: <http://www.dsireusa.org/>

See also [www.ncsl.org/research/energy/renewable-portfolio-standards.aspx](http://www.ncsl.org/research/energy/renewable-portfolio-standards.aspx)

# Interconnected Power System

## Basic Characteristics

---



- Three – phase AC systems:
  - generation and transmission equipment is usually three phase
  - industrial loads are three phase
  - residential and commercial loads are single phase and distributed equally among the phases; consequently, a balanced three – phase system results
- Synchronous machines have traditionally generated electricity, though this is rapidly changing with the addition of more inverter-connected generation (such as solar and most wind)
- Interconnection transmits power over a wider region with subsystems operating at different voltage levels



# Quick Review of Per Unit (From Undergrad Class)

---



- A key problem in analyzing power systems is the large number of transformers.
  - It would be very difficult to continually have to refer impedances to the different sides of the transformers
- This problem is avoided by a normalization of all variables.
- This normalization is known as per unit analysis.

$$\text{quantity in per unit} = \frac{\text{actual quantity}}{\text{base value of quantity}}$$

# Per Unit Conversion Procedure, Single-Phase

---



1. Pick a 1 $\phi$  VA base for the entire system,  $S_B$
2. Pick a voltage base for each different voltage level,  $V_B$ . Voltage bases are related by transformer turns ratios. Voltages are line to neutral.
3. Calculate the impedance base,  $Z_B = (V_B)^2/S_B$
4. Calculate the current base,  $I_B = V_B/Z_B$
5. Convert actual values to per unit

Note, per unit conversion on affects magnitudes, not the angles. Also, per unit quantities no longer have units (i.e., a voltage is 1.0 p.u., not 1 p.u. volts)

# Per Unit Solution Procedure


---



1. Convert to per unit (p.u.) (many problems are already in per unit)
2. Solve
3. Convert back to actual as necessary
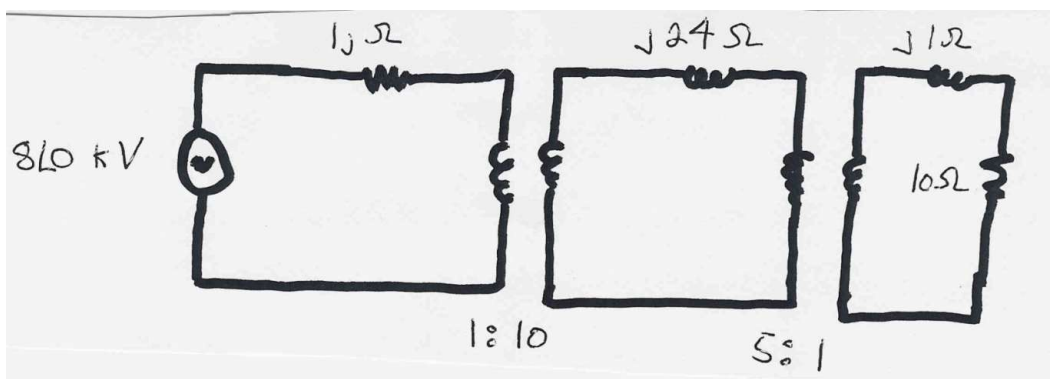
# Per Unit Example


- Solve for the current, load voltage and load power in the circuit shown below using per unit analysis with an  $S_B$  of 100 MVA, and voltage bases of 8 kV, 80 kV and 16 kV



$$Z_B^{Left} = \frac{8kV^2}{100MVA} = 0.64\Omega$$

$$Z_B^{Middle} = \frac{80kV^2}{100MVA} = 64\Omega$$
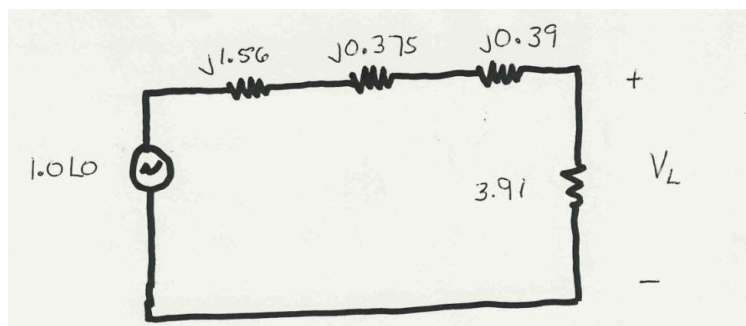
$$Z_B^{Right} = \frac{16kV^2}{100MVA} = 2.56\Omega$$



Same circuit, with values expressed in per unit.

## Per Unit Example, cont'd




$$I = \frac{1.0 \angle 0^\circ}{3.91 + j2.327} = 0.22 \angle -30.8^\circ \text{ p.u. (not amps)}$$

$$\begin{aligned} V_L &= 1.0 \angle 0^\circ - 0.22 \angle -30.8^\circ \times 2.327 \angle 90^\circ \\ &= 0.859 \angle -30.8^\circ \text{ p.u.} \end{aligned}$$

$$S_L = V_L I_L^* = \frac{|V_L|^2}{Z} = 0.189 \text{ p.u.}$$
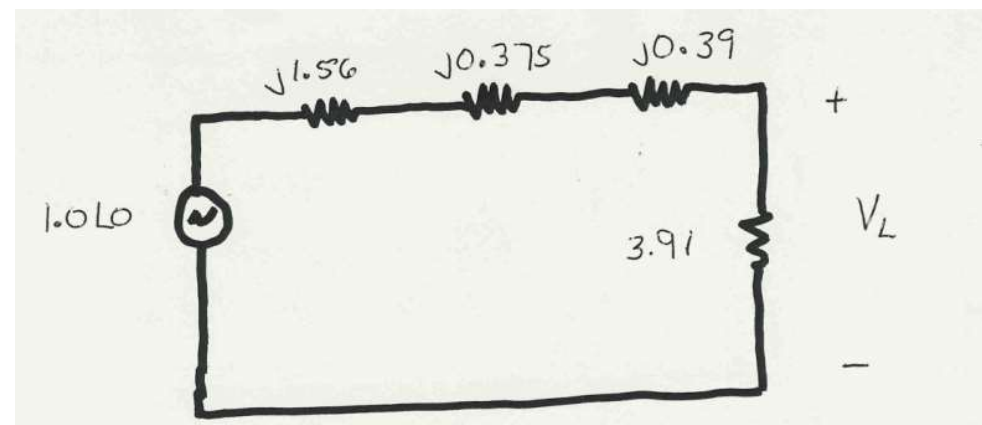
$$S_G = 1.0 \angle 0^\circ \times 0.22 \angle 30.8^\circ = 0.22 \angle 30.8^\circ \text{ p.u.}$$



## Per Unit Example, cont'd



- To convert back to actual values just multiply the per unit values by their per unit base

$$V_L^{\text{Actual}} = 0.859 \angle -30.8^\circ \times 16 \text{ kV} = 13.7 \angle -30.8^\circ \text{ kV}$$

$$S_L^{\text{Actual}} = 0.189 \angle 0^\circ \times 100 \text{ MVA} = 18.9 \angle 0^\circ \text{ MVA}$$

$$S_G^{\text{Actual}} = 0.22 \angle 30.8^\circ \times 100 \text{ MVA} = 22.0 \angle 30.8^\circ \text{ MVA}$$

$$I_B^{\text{Middle}} = \frac{100 \text{ MVA}}{80 \text{ kV}} = 1250 \text{ Amps}$$

$$I_{\text{Middle}}^{\text{Actual}} = 0.22 \angle -30.8^\circ \times 1250 \text{ Amps} = 275 \angle -30.8^\circ \text{ A}$$

# Procedure for Balanced Three-Phase Circuits



Procedure is very similar to 1 $\phi$  except we use a 3 $\phi$  VA base, and use line to line voltage bases

1. Pick a 3 $\phi$  VA base for the entire system,
2. Pick a voltage base for each different voltage level,  $V_B$ . Voltages are line to line.
3. Calculate the impedance base

$$Z_B = \frac{V_{B,LL}^2}{S_B^{3\phi}} = \frac{(\sqrt{3} V_{B,LN})^2}{3S_B^{1\phi}} = \frac{V_{B,LN}^2}{S_B^{1\phi}}$$

Exactly the same impedance bases as with single phase!

## Three-Phase Per Unit, cont'd

---



4. Calculate the current base,  $I_B$

$$I_B^{3\phi} = \frac{S_B^{3\phi}}{\sqrt{3} V_{B,LL}} = \frac{3 S_B^{1\phi}}{\sqrt{3} \sqrt{3} V_{B,LN}} = \frac{S_B^{1\phi}}{V_{B,LN}} = I_B^{1\phi}$$


5. Convert actual values to per unit


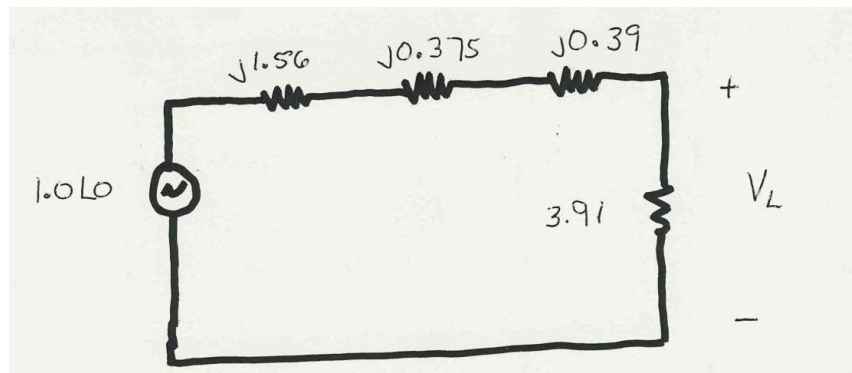
# Three-Phase Per Unit Example



Solve for the current, load voltage and load power in the previous circuit, assuming a 3 $\phi$  power base of **300 MVA**, and line to line voltage bases of 13.8 kV, 138 kV and 27.6 kV (square root of 3 larger than the 1 $\phi$  example voltages). Also assume the generator is Y-connected so its line to line voltage is 13.8 kV.



Convert to per unit as before. Note the system is exactly the same!

## Three-Phase Per Unit Example, cont.



$$I = \frac{1.0 \angle 0^\circ}{3.91 + j2.327} = 0.22 \angle -30.8^\circ \text{ p.u. (not amps)}$$

$$\begin{aligned} V_L &= 1.0 \angle 0^\circ - 0.22 \angle -30.8^\circ \times 2.327 \angle 90^\circ \\ &= 0.859 \angle -30.8^\circ \text{ p.u.} \end{aligned}$$

$$S_L = V_L I_L^* = \frac{|V_L|^2}{Z} = 0.189 \text{ p.u.}$$

Again, analysis is exactly the same!

$$S_G = 1.0 \angle 0^\circ \times 0.22 \angle 30.8^\circ = 0.22 \angle 30.8^\circ \text{ p.u.}$$

## Three-Phase Per Unit Example, cont'd



- Differences appear when we convert back to actual values

$$V_L^{\text{Actual}} = 0.859 \angle -30.8^\circ \times 27.6 \text{ kV} = 23.8 \angle -30.8^\circ \text{ kV}$$

$$S_L^{\text{Actual}} = 0.189 \angle 0^\circ \times 300 \text{ MVA} = 56.7 \angle 0^\circ \text{ MVA}$$

$$S_G^{\text{Actual}} = 0.22 \angle 30.8^\circ \times 300 \text{ MVA} = 66.0 \angle 30.8^\circ \text{ MVA}$$


$$I_B^{\text{Middle}} = \frac{300 \text{ MVA}}{\sqrt{3} 138 \text{ kV}} = 1250 \text{ Amps} \quad (\text{same current!})$$

$$I_{\text{Middle}}^{\text{Actual}} = 0.22 \angle -30.8^\circ \times 1250 \text{ Amps} = 275 \angle -30.8^\circ \text{ A}$$
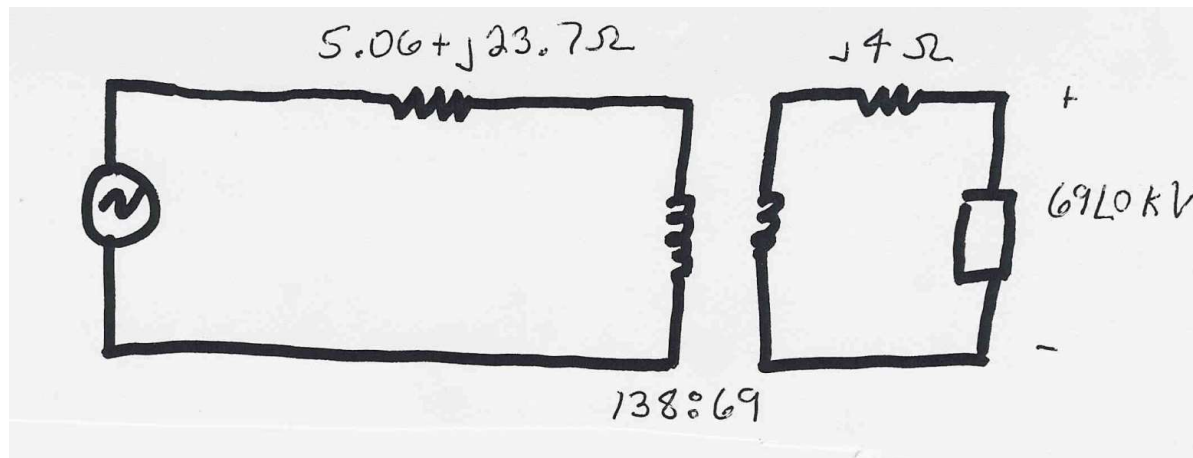
## Three-Phase Per Unit Example 2



- Assume a 3 $\phi$  load of  $100+j50$  MVA with  $V_{LL}$  of 69 kV is connected to a source through the below network:



What is the supply current and complex power?

Answer:  $I=467$  amps,  $S = 103.3 + j76.0$  MVA

# Power Flow Analysis

---



- We now have the necessary models to start to develop the power system analysis tools
- The most common power system analysis tool is the power flow (also known sometimes as the load flow)
  - power flow determines how the power flows in a network
  - also used to determine all bus voltages and all currents
  - because of constant power models, power flow is a nonlinear analysis technique
  - power flow is a steady-state analysis tool

# Linear versus Nonlinear Systems

---



A function  $\mathbf{H}$  is linear if

$$\mathbf{H}(\alpha_1 \mu_1 + \alpha_2 \mu_2) = \alpha_1 \mathbf{H}(\mu_1) + \alpha_2 \mathbf{H}(\mu_2)$$

That is

- 1) the output is proportional to the input
- 2) the principle of superposition holds

**Linear Example:**  $y = \mathbf{H}(\mathbf{x}) = c \mathbf{x}$

$$y = c(\mathbf{x}_1 + \mathbf{x}_2) = c\mathbf{x}_1 + c \mathbf{x}_2$$

**Nonlinear Example:**  $y = \mathbf{H}(\mathbf{x}) = c \mathbf{x}^2$

$$y = c(\mathbf{x}_1 + \mathbf{x}_2)^2 \neq (c\mathbf{x}_1)^2 + (c \mathbf{x}_2)^2$$


# Linear Power System Elements



Resistors, inductors, capacitors, independent voltage sources and current sources are linear circuit elements


$$V = R I \quad V = j\omega L I \quad V = \frac{1}{j\omega C} I$$

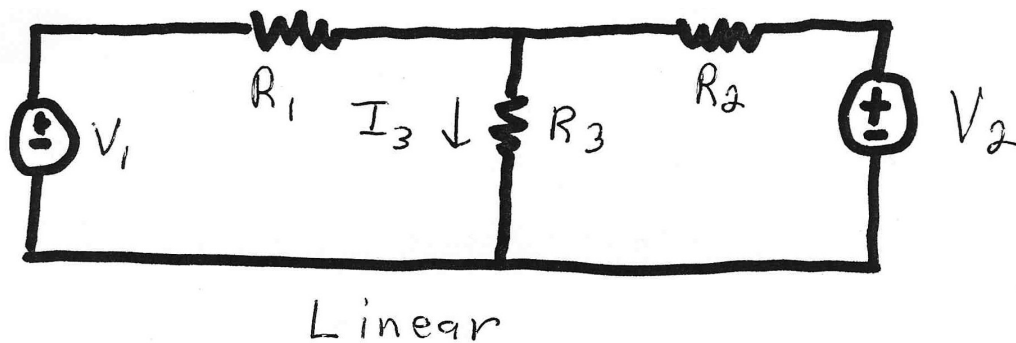Such systems may be analyzed by superposition


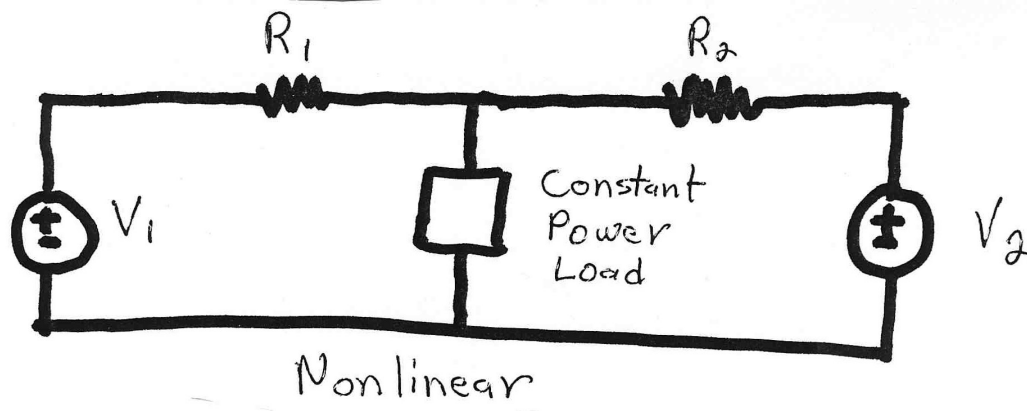
# Nonlinear System Example

- Constant power loads and generator injections are nonlinear and hence systems with these elements can not be analyzed by superposition



Nonlinear problems can be very difficult to solve, and usually require an iterative approach




# Nonlinear Systems May Have Multiple Solutions or No Solution

Example 1:  $x^2 - 2 = 0$  has solutions  $x = \pm 1.414\dots$

Example 2:  $x^2 + 2 = 0$  has no real solution

$$f(x) = x^2 - 2$$

$$f(x) = x^2 + 2$$

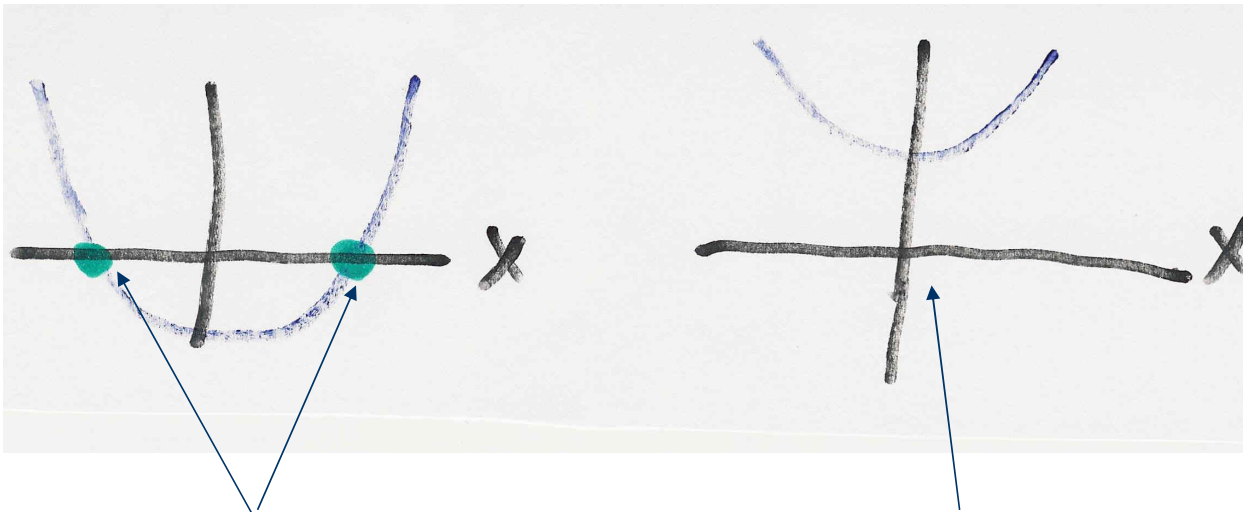


two solutions where  $f(x) = 0$

no solution  $f(x) = 0$
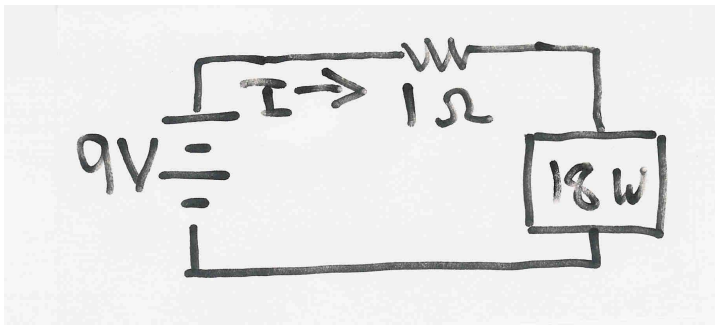
# Multiple Solution Example



- The dc system shown below has two solutions:



where the 18 watt load is a resistive load

What is the maximum  $P_{Load}$ ?

The equation we're solving is

$$I^2 R_{Load} = \left( \frac{9 \text{ volts}}{1\Omega + R_{Load}} \right)^2 R_{Load} = 18 \text{ watts}$$

One solution is  $R_{Load} = 2\Omega$

Other solution is  $R_{Load} = 0.5\Omega$

# Bus Admittance Matrix or $Y_{bus}$

---




- First step in solving the power flow is to create what is known as the bus admittance matrix, often call the  $Y_{bus}$ .
- The  $Y_{bus}$  gives the relationships between all the bus current injections,  $I$ , and all the bus voltages,  $V$ ,
$$I = Y_{bus} V$$
- The  $Y_{bus}$  is developed by applying KCL at each bus in the system to relate the bus current injections, the bus voltages, and the branch impedances and admittances
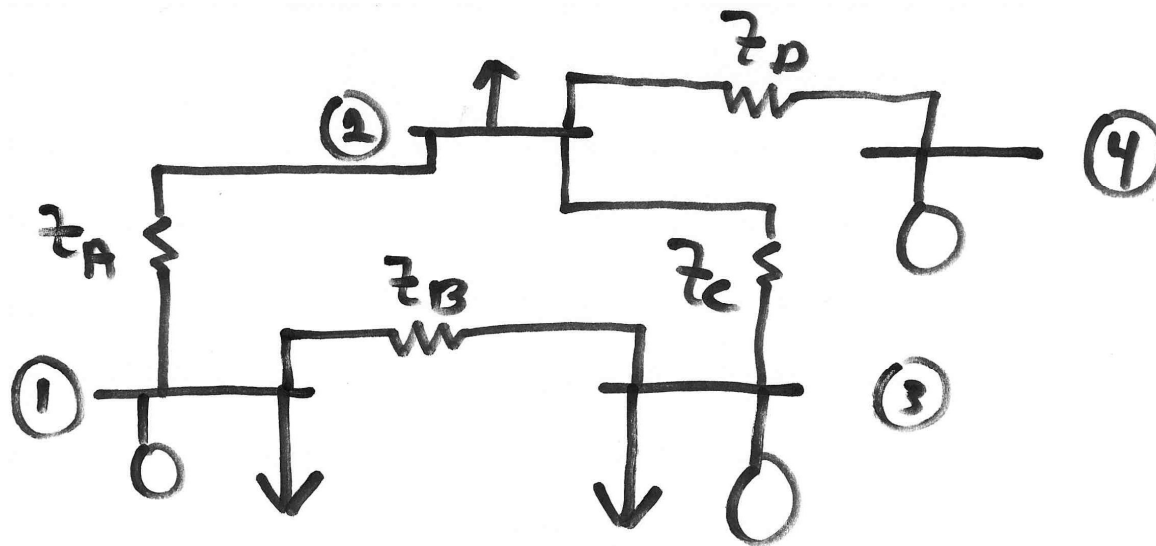
## $Y_{\text{bus}}$ Example



Determine the bus admittance matrix for the network shown below, assuming the current injection at each bus  $i$  is  $I_i = I_{Gi} - I_{Di}$  where  $I_{Gi}$  is the current injection into the bus from the generator and  $I_{Di}$  is the current flowing into the load



## $Y_{\text{bus}}$ Example, cont'd



By KCL at bus 1 we have

$$I_1 = I_{G1} - I_{D1}$$

$$I_1 = I_{12} + I_{13} = \frac{V_1 - V_2}{Z_A} + \frac{V_1 - V_3}{Z_B}$$

$$I_1 = (V_1 - V_2)Y_A + (V_1 - V_3)Y_B \quad (\text{with } Y_j = \frac{1}{Z_j})$$

$$= (Y_A + Y_B)V_1 - Y_A V_2 - Y_B V_3$$

Similarly

$$I_2 = I_{21} + I_{23} + I_{24}$$

$$= -Y_A V_1 + (Y_A + Y_C + Y_D)V_2 - Y_C V_3 - Y_D V_4$$

## $Y_{bus}$ Example, cont'd



We can get similar relationships for buses 3 and 4

The results can then be expressed in matrix form

$$\mathbf{I} = \mathbf{Y}_{bus} \mathbf{V}$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} Y_A + Y_B & -Y_A & -Y_B & 0 \\ -Y_A & Y_A + Y_C + Y_D & -Y_C & -Y_D \\ -Y_B & -Y_C & Y_B + Y_C & 0 \\ 0 & -Y_D & 0 & Y_D \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}$$

For a system with  $n$  buses the  $Y_{bus}$  is an  $n$  by  $n$  symmetric matrix (i.e., one where  $A_{ij} = A_{ji}$ ); however this will not be true in general when we consider phase shifting transformers

# $Y_{bus}$ General Form

---



- The diagonal terms,  $Y_{ii}$ , are the self admittance terms, equal to the sum of the admittances of all devices incident to bus  $i$ .
- The off-diagonal terms,  $Y_{ij}$ , are equal to the negative of the sum of the admittances joining the two buses.
- With large systems  $Y_{bus}$  is a sparse matrix (that is, most entries are zero)
- Shunt terms, such as with the  $\pi$  line model, only affect the diagonal terms.