

ECEN 615

Methods of Electric Power Systems Analysis

Lecture 3: Per Unit, Ybus, Power Flow

Prof. Tom Overbye

Dept. of Electrical and Computer Engineering

Texas A&M University

overbye@tamu.edu



TEXAS A&M
UNIVERSITY

Announcements



- Start reading Chapter 6 from the book
- Homework 1 is assigned today. It is due on Thursday Sept. 13

Load Models (Omitted from Lecture 2)



- Ultimate goal is to supply loads with electricity at constant frequency and voltage
- Electrical characteristics of individual loads matter, but usually they can only be estimated
 - actual loads are constantly changing, consisting of a large number of individual devices
 - only limited network observability of load characteristics
- Aggregate models are typically used for analysis
- Two common models
 - constant power: $S_i = P_i + jQ_i$
 - constant impedance: $S_i = |V|^2 / Z_i$

The ZIP model combines constant impedance, current and power (P)

Three-Phase Per Unit



Procedure is very similar to 1 ϕ except we use a 3 ϕ VA base, and use line to line voltage bases

1. Pick a 3 ϕ VA base for the entire system,
2. Pick a voltage base for each different voltage level, V_B . Voltages are line to line.
3. Calculate the impedance base

$$Z_B = \frac{V_{B,LL}^2}{S_B^{3\phi}} = \frac{(\sqrt{3} V_{B,LN})^2}{3S_B^{1\phi}} = \frac{V_{B,LN}^2}{S_B^{1\phi}}$$

Exactly the same impedance bases as with single phase!

Three-Phase Per Unit, cont'd



4. Calculate the current base, I_B

$$I_B^{3\phi} = \frac{S_B^{3\phi}}{\sqrt{3} V_{B,LL}} = \frac{3 S_B^{1\phi}}{\sqrt{3} \sqrt{3} V_{B,LN}} = \frac{S_B^{1\phi}}{V_{B,LN}} = I_B^{1\phi}$$


Exactly the same current bases as with single-phase!

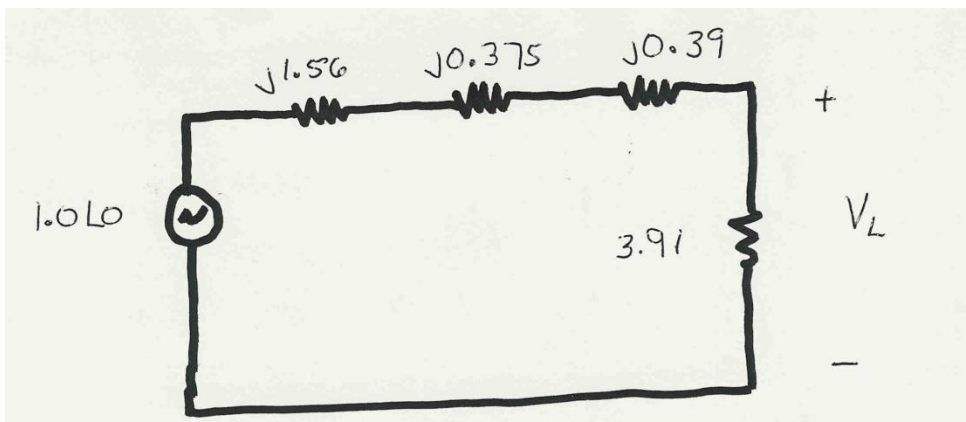5. Convert actual values to per unit

Three-Phase Per Unit Example



Solve for the current, load voltage and load power in the previous circuit, assuming a 3 ϕ power base of **300 MVA**, and line to line voltage bases of 13.8 kV, 138 kV and 27.6 kV (square root of 3 larger than the 1 ϕ example voltages). Also assume the generator is Y-connected so its line to line voltage is 13.8 kV.



Convert to per unit as before. Note the system is exactly the same!

Three-Phase Per Unit Example, cont.



$$I = \frac{1.0 \angle 0^\circ}{3.91 + j2.327} = 0.22 \angle -30.8^\circ \text{ p.u. (not amps)}$$

$$\begin{aligned} V_L &= 1.0 \angle 0^\circ - 0.22 \angle -30.8^\circ \times 2.327 \angle 90^\circ \\ &= 0.859 \angle -30.8^\circ \text{ p.u.} \end{aligned}$$

$$S_L = V_L I_L^* = \frac{|V_L|^2}{Z} = 0.189 \text{ p.u.}$$

$$S_G = 1.0 \angle 0^\circ \times 0.22 \angle 30.8^\circ = 0.22 \angle 30.8^\circ \text{ p.u.}$$

Again, analysis is exactly the same!

Three-Phase Per Unit Example, cont'd



Differences appear when we convert back to actual values

$$V_L^{\text{Actual}} = 0.859 \angle -30.8^\circ \times 27.6 \text{ kV} = 23.8 \angle -30.8^\circ \text{ kV}$$

$$S_L^{\text{Actual}} = 0.189 \angle 0^\circ \times 300 \text{ MVA} = 56.7 \angle 0^\circ \text{ MVA}$$

$$S_G^{\text{Actual}} = 0.22 \angle 30.8^\circ \times 300 \text{ MVA} = 66.0 \angle 30.8^\circ \text{ MVA}$$


$$I_B^{\text{Middle}} = \frac{300 \text{ MVA}}{\sqrt{3} 138 \text{ kV}} = 1250 \text{ Amps} \quad (\text{same current!})$$

$$I_{\text{Middle}}^{\text{Actual}} = 0.22 \angle -30.8^\circ \times 1250 \text{ Amps} = 275 \angle -30.8^\circ \text{ A}$$

Three-Phase Per Unit Example 2



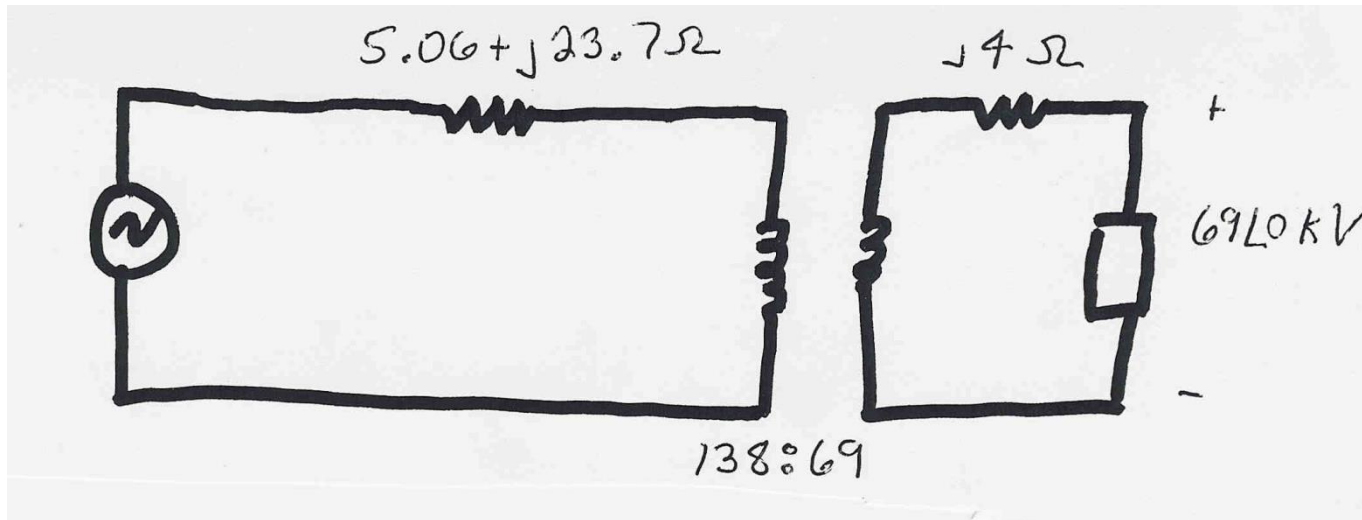- Assume a 3 ϕ load of $100+j50$ MVA with V_{LL} of 69 kV is connected to a source through the below network:



What is the supply current and complex power?

Answer: $I=467$ amps, $S = 103.3 + j76.0$ MVA

Power Flow Analysis



- We now have the necessary models to start to develop the power system analysis tools
- The most common power system analysis tool is the power flow (also known sometimes as the load flow)
 - power flow determines how the power flows in a network
 - also used to determine all bus voltages and all currents
 - because of constant power models, power flow is a nonlinear analysis technique
 - power flow is a steady-state analysis tool

Linear versus Nonlinear Systems



A function \mathbf{H} is linear if

$$\mathbf{H}(\alpha_1 \boldsymbol{\mu}_1 + \alpha_2 \boldsymbol{\mu}_2) = \alpha_1 \mathbf{H}(\boldsymbol{\mu}_1) + \alpha_2 \mathbf{H}(\boldsymbol{\mu}_2)$$

That is

- 1) the output is proportional to the input
- 2) the principle of superposition holds

Linear Example: $y = \mathbf{H}(\mathbf{x}) = c \mathbf{x}$

$$y = c(\mathbf{x}_1 + \mathbf{x}_2) = c\mathbf{x}_1 + c \mathbf{x}_2$$

Nonlinear Example: $y = \mathbf{H}(\mathbf{x}) = c \mathbf{x}^2$

$$y = c(\mathbf{x}_1 + \mathbf{x}_2)^2 \neq (c\mathbf{x}_1)^2 + (c \mathbf{x}_2)^2$$


Linear Power System Elements



Resistors, inductors, capacitors, independent voltage sources and current sources are linear circuit elements


$$V = R I \quad V = j\omega L I \quad V = \frac{1}{j\omega C} I$$

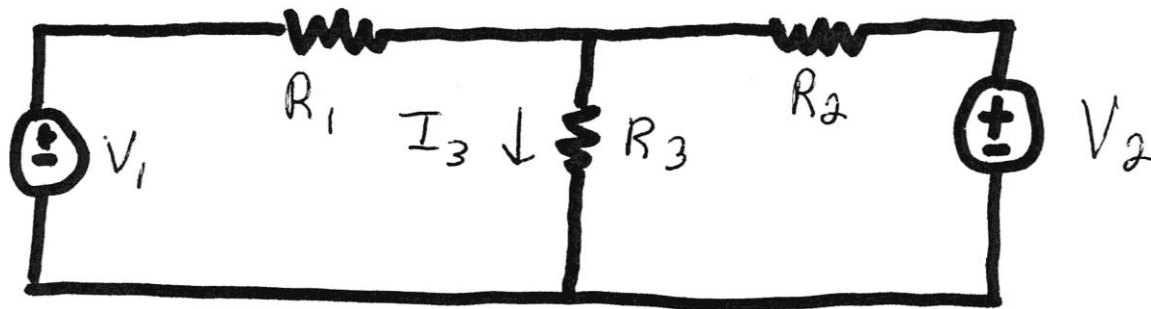Such systems may be analyzed by superposition



Linear

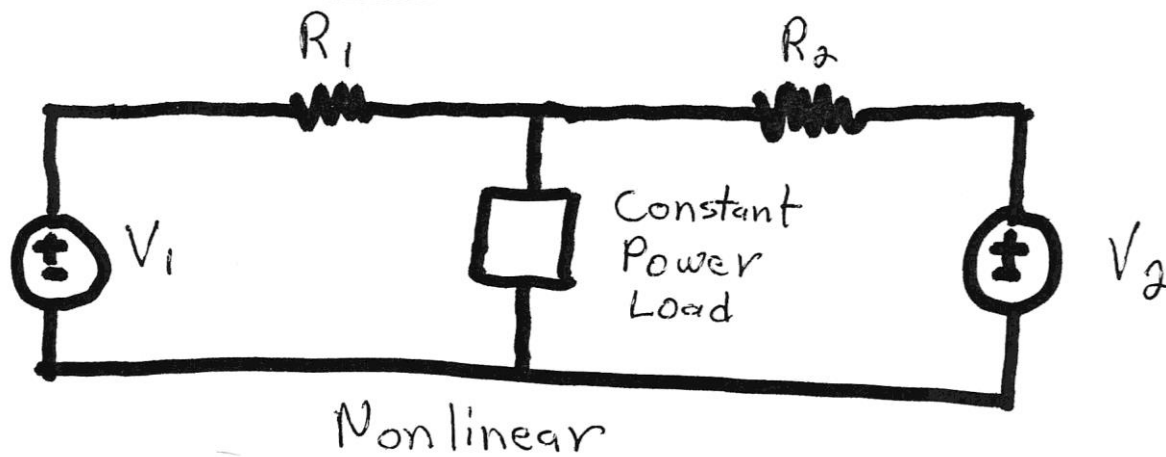- Constant power loads and generator injections are nonlinear and hence systems with these elements can not be analyzed by superposition



Nonlinear problems can be very difficult to solve, and usually require an iterative approach

Nonlinear Systems May Have Multiple Solutions or No Solution




Example 1: $x^2 - 2 = 0$ has solutions $x = \pm 1.414\dots$

Example 2: $x^2 + 2 = 0$ has no real solution

$$f(x) = x^2 - 2$$

$$f(x) = x^2 + 2$$

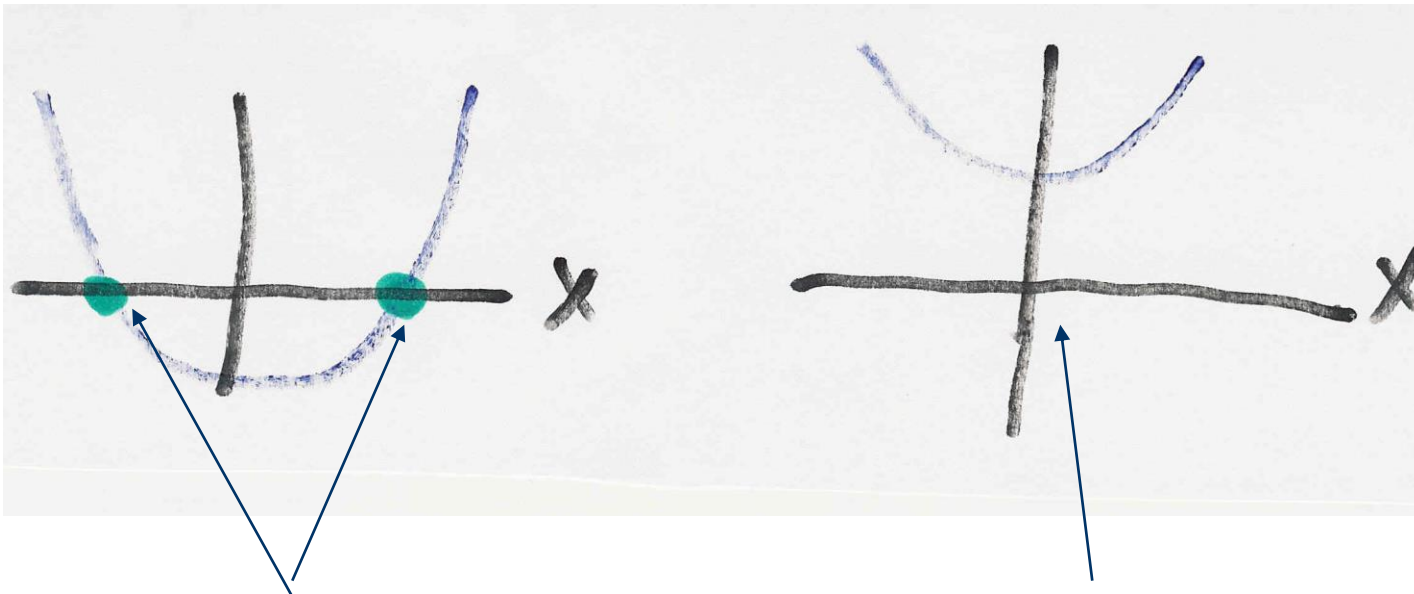


two solutions where $f(x) = 0$

no solution $f(x) = 0$

Multiple Solution Example

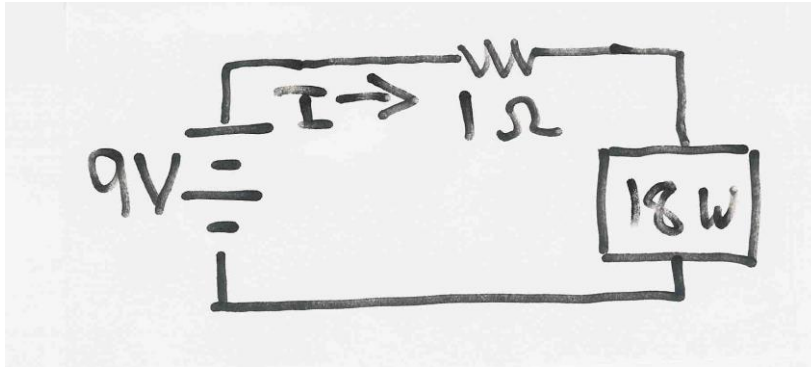- The dc system shown below has two solutions:



where the 18 watt load is a resistive load

The equation we're solving is

$$I^2 R_{Load} = \left(\frac{9 \text{ volts}}{1\Omega + R_{Load}} \right)^2 R_{Load} = 18 \text{ watts}$$

One solution is $R_{Load} = 2\Omega$

Other solution is $R_{Load} = 0.5\Omega$

What is the maximum P_{Load} ?

Bus Admittance Matrix or Y_{bus}




- First step in solving the power flow is to create what is known as the bus admittance matrix, often call the Y_{bus} .
- The Y_{bus} gives the relationships between all the bus current injections, \mathbf{I} , and all the bus voltages, \mathbf{V} ,
$$\mathbf{I} = \mathbf{Y}_{bus} \mathbf{V}$$
- The Y_{bus} is developed by applying KCL at each bus in the system to relate the bus current injections, the bus voltages, and the branch impedances and admittances

Y_{bus} Example



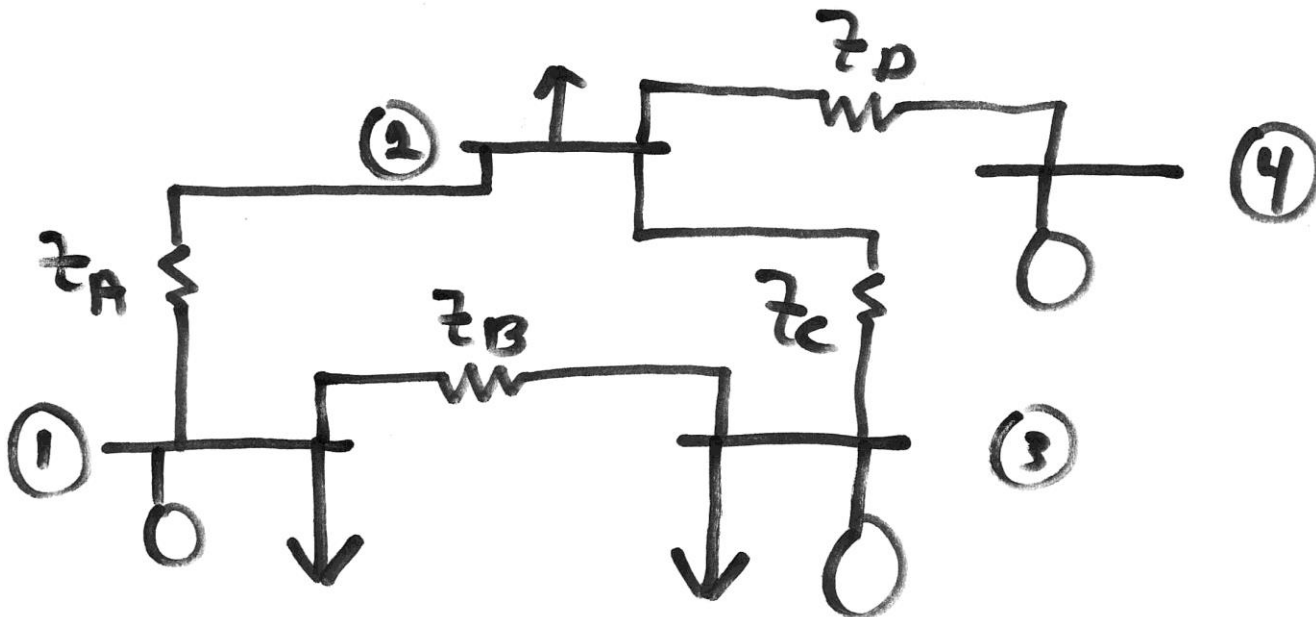Determine the bus admittance matrix for the network shown below, assuming the current injection at each bus i is $I_i = I_{Gi} - I_{Di}$ where I_{Gi} is the current injection into the bus from the generator and I_{Di} is the current flowing into the load



Y_{bus} Example, cont'd



By KCL at bus 1 we have

$$I_1 \triangleq I_{G1} - I_{D1}$$

$$I_1 = I_{12} + I_{13} = \frac{V_1 - V_2}{Z_A} + \frac{V_1 - V_3}{Z_B}$$

$$I_1 = (V_1 - V_2)Y_A + (V_1 - V_3)Y_B \quad (\text{with } Y_j = \frac{1}{Z_j})$$

$$= (Y_A + Y_B)V_1 - Y_A V_2 - Y_B V_3$$

Similarly

$$I_2 = I_{21} + I_{23} + I_{24}$$

$$= -Y_A V_1 + (Y_A + Y_C + Y_D)V_2 - Y_C V_3 - Y_D V_4$$

Y_{bus} Example, cont'd



We can get similar relationships for buses 3 and 4

The results can then be expressed in matrix form

$$\mathbf{I} = \mathbf{Y}_{bus} \mathbf{V}$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} Y_A + Y_B & -Y_A & -Y_B & 0 \\ -Y_A & Y_A + Y_C + Y_D & -Y_C & -Y_D \\ -Y_B & -Y_C & Y_B + Y_C & 0 \\ 0 & -Y_D & 0 & Y_D \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}$$


For a system with n buses the Y_{bus} is an n by n symmetric matrix (i.e., one where $A_{ij} = A_{ji}$); however this will not be true in general when we consider phase shifting transformers

Y_{bus} General Form



- The diagonal terms, Y_{ii} , are the self admittance terms, equal to the sum of the admittances of all devices incident to bus i .
- The off-diagonal terms, Y_{ij} , are equal to the negative of the sum of the admittances joining the two buses.
- With large systems Y_{bus} is a sparse matrix (that is, most entries are zero)
- Shunt terms, such as with the π line model, only affect the diagonal terms.

Modeling Shunts in the Y_{bus}

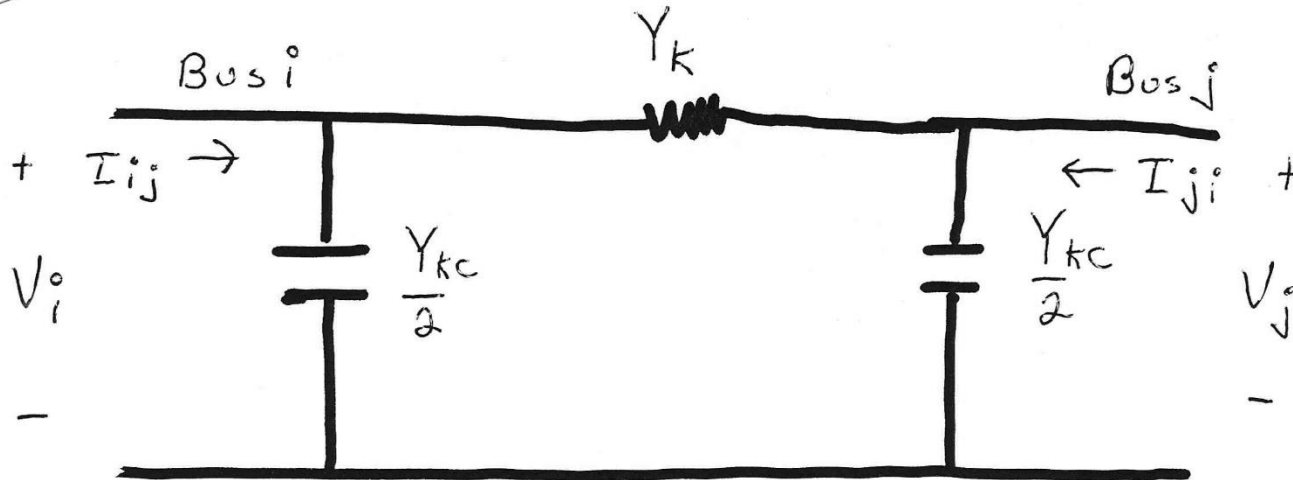

Since
$$I_{ij} = (V_i - V_j)Y_k + V_i \frac{Y_{kc}}{2}$$


$$Y_{ii} = Y_{ii}^{\text{from other lines}} + Y_k + \frac{Y_{kc}}{2}$$

Note
$$Y_k = \frac{1}{Z_k} = \frac{1}{R_k + jX_k} \frac{R_k - jX_k}{R_k - jX_k} = \frac{R_k - jX_k}{R_k^2 + X_k^2}$$

Two Bus System Example



Two Bus Example

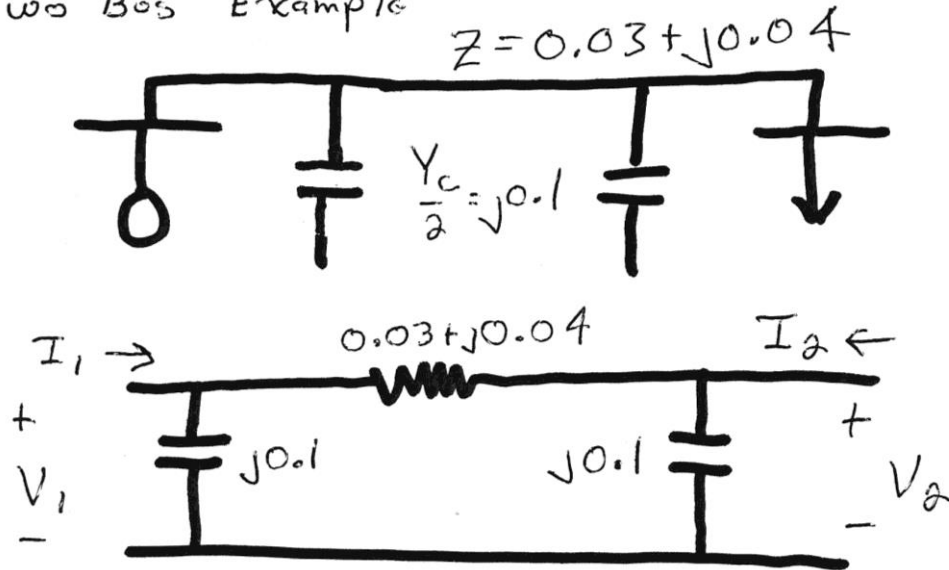

$$I_1 = \frac{(V_1 - V_2)}{Z} + V_1 \frac{Y_c}{2} = \frac{1}{0.03 + j0.04} = 12 - j16$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 - j15.9 & -12 + j16 \\ -12 + j16 & 12 - j15.9 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Using the \mathbf{Y}_{bus}



If the voltages are known then we can solve for the current injections:

$$\mathbf{Y}_{bus} \mathbf{V} = \mathbf{I}$$

If the current injections are known then we can solve for the voltages:

$$\mathbf{Y}_{bus}^{-1} \mathbf{I} = \mathbf{V} = \mathbf{Z}_{bus} \mathbf{I}$$

where \mathbf{Z}_{bus} is the bus impedance matrix

However, this requires that \mathbf{Y}_{bus} not be singular; note it will be singular if there are no shunt connections!

Solving for Bus Currents



For example, in previous case assume

$$\mathbf{V} = \begin{bmatrix} 1.0 \\ 0.8 - j0.2 \end{bmatrix}$$

Then

$$\begin{bmatrix} 12 - j15.9 & -12 + j16 \\ -12 + j16 & 12 - j15.9 \end{bmatrix} \begin{bmatrix} 1.0 \\ 0.8 - j0.2 \end{bmatrix} = \begin{bmatrix} 5.60 - j0.70 \\ -5.58 + j0.88 \end{bmatrix}$$

Therefore the power injected at bus 1 is

$$S_1 = V_1 I_1^* = 1.0 \times (5.60 + j0.70) = 5.60 + j0.70$$

$$S_2 = V_2 I_2^* = (0.8 - j0.2) \times (-5.58 - j0.88) = -4.64 + j0.41$$

Solving for Bus Voltages



For example, in previous case assume

$$\mathbf{I} = \begin{bmatrix} 5.0 \\ -4.8 \end{bmatrix}$$

Then

$$\begin{bmatrix} 12 - j15.9 & -12 + j16 \\ -12 + j16 & 12 - j15.9 \end{bmatrix}^{-1} \begin{bmatrix} 5.0 \\ -4.8 \end{bmatrix} = \begin{bmatrix} 0.0738 - j0.902 \\ -0.0738 - j1.098 \end{bmatrix}$$

Therefore the power injected is

$$S_1 = V_1 I_1^* = (0.0738 - j0.902) \times 5 = 0.37 - j4.51$$

$$S_2 = V_2 I_2^* = (-0.0738 - j1.098) \times (-4.8) = 0.35 + j5.27$$

Power Flow Analysis



- When analyzing power systems we know neither the complex bus voltages nor the complex current injections
- Rather, we know the complex power being consumed by the load, and the power being injected by the generators plus their voltage magnitudes
- Therefore we can not directly use the Y_{bus} equations, but rather must use the power balance equations

Power Balance Equations



From KCL we know at each bus i in an n bus system the current injection, I_i , must be equal to the current that flows into the network

$$I_i = I_{Gi} - I_{Di} = \sum_{k=1}^n I_{ik}$$

Since $\mathbf{I} = \mathbf{Y}_{\text{bus}} \mathbf{V}$ we also know

$$I_i = I_{Gi} - I_{Di} = \sum_{k=1}^n Y_{ik} V_k$$

The network power injection is then $S_i = V_i I_i^*$

Power Balance Equations, cont'd



$$S_i = V_i I_i^* = V_i \left(\sum_{k=1}^n Y_{ik} V_k \right)^* = V_i \sum_{k=1}^n Y_{ik}^* V_k^*$$

This is an equation with complex numbers.

Sometimes we would like an equivalent set of real power equations. These can be derived by defining

$$Y_{ik} \triangleq G_{ik} + jB_{ik}$$

$$V_i \triangleq |V_i| e^{j\theta_i} = |V_i| \angle \theta_i$$

$$\theta_{ik} \triangleq \theta_i - \theta_k$$

Recall $e^{j\theta} = \cos \theta + j \sin \theta$

Real Power Balance Equations



$$\begin{aligned} S_i &= P_i + jQ_i = V_i \sum_{k=1}^n Y_{ik}^* V_k^* = \sum_{k=1}^n |V_i| |V_k| e^{j\theta_{ik}} (G_{ik} - jB_{ik}) \\ &= \sum_{k=1}^n |V_i| |V_k| (\cos \theta_{ik} + j \sin \theta_{ik}) (G_{ik} - jB_{ik}) \end{aligned}$$

Resolving into the real and imaginary parts

$$P_i = \sum_{k=1}^n |V_i| |V_k| (G_{ik} \cos \theta_{ik} + B_{ik} \sin \theta_{ik}) = P_{Gi} - P_{Di}$$

$$Q_i = \sum_{k=1}^n |V_i| |V_k| (G_{ik} \sin \theta_{ik} - B_{ik} \cos \theta_{ik}) = Q_{Gi} - Q_{Di}$$

Power Flow Analysis



- When analyzing power systems we know neither the complex bus voltages nor the complex current injections
- Rather, we know the complex power being consumed by the load, and the power being injected by the generators plus their voltage magnitudes
- Therefore we can not directly use the Y_{bus} equations, but rather must use the power balance equations

Power Flow Analysis



- Classic paper for this lecture is W.F. Tinney and C.E. Hart, “Power Flow Solution by Newton’s Method,” IEEE Power App System, Nov 1967
- Basic power flow is also covered in essentially power system analysis textbooks.
- We use the term “power flow” not “load flow” since power flows not load. Also, the power flow usage is not new (see title of Tinney’s 1967 paper, and note Tinney references Ward’s 1956 paper)
 - A nice history of the power flow is given in an insert by Alvarado and Thomas in T.J. Overbye, J.D. Weber, “Visualizing the Electric Grid,” *IEEE Spectrum*, Feb 2001.

Power Balance Equations



From KCL we know at each bus i in an n bus system the current injection, I_i , must be equal to the current that flows into the network

$$I_i = I_{Gi} - I_{Di} = \sum_{k=1}^n I_{ik}$$

Since $\mathbf{I} = \mathbf{Y}_{\text{bus}} \mathbf{V}$ we also know

$$I_i = I_{Gi} - I_{Di} = \sum_{k=1}^n Y_{ik} V_k$$

The network power injection is then $S_i = V_i I_i^*$

Power Balance Equations, cont'd



$$S_i = V_i I_i^* = V_i \left(\sum_{k=1}^n Y_{ik} V_k \right)^* = V_i \sum_{k=1}^n Y_{ik}^* V_k^*$$

This is an equation with complex numbers.

Sometimes we would like an equivalent set of real power equations. These can be derived by defining

$$Y_{ik} \triangleq G_{ik} + jB_{ik}$$

$$V_i \triangleq |V_i| e^{j\theta_i} = |V_i| \angle \theta_i$$

$$\theta_{ik} \triangleq \theta_i - \theta_k$$

Recall $e^{j\theta} = \cos \theta + j \sin \theta$

These equations can also be formulated using rectangular coordinates for the voltages:

$$V_i = e_i + jf_i$$

Real Power Balance Equations



$$\begin{aligned} S_i &= P_i + jQ_i = V_i \sum_{k=1}^n Y_{ik}^* V_k^* = \sum_{k=1}^n |V_i| |V_k| e^{j\theta_{ik}} (G_{ik} - jB_{ik}) \\ &= \sum_{k=1}^n |V_i| |V_k| (\cos \theta_{ik} + j \sin \theta_{ik}) (G_{ik} - jB_{ik}) \end{aligned}$$

Resolving into the real and imaginary parts

$$P_i = \sum_{k=1}^n |V_i| |V_k| (G_{ik} \cos \theta_{ik} + B_{ik} \sin \theta_{ik}) = P_{Gi} - P_{Di}$$

$$Q_i = \sum_{k=1}^n |V_i| |V_k| (G_{ik} \sin \theta_{ik} - B_{ik} \cos \theta_{ik}) = Q_{Gi} - Q_{Di}$$

Slack Bus



- We can not arbitrarily specify S at all buses because total generation must equal total load + total losses
- We also need an angle reference bus.
- To solve these problems we define one bus as the "slack" bus. This bus has a fixed voltage magnitude and angle, and a varying real/reactive power injection.
- In an actual power system the slack bus does not really exist; frequency changes locally when the power supplied does not match the power consumed

Three Types of Power Flow Buses



- There are three main types of power flow buses
 - Load (PQ) at which P/Q are fixed; iteration solves for voltage magnitude and angle.
 - Slack at which the voltage magnitude and angle are fixed; iteration solves for P/Q injections
 - Generator (PV) at which P and $|V|$ are fixed; iteration solves for voltage angle and Q injection

Newton-Raphson Algorithm



- Most common technique for solving the power flow problem is to use the Newton-Raphson algorithm
- Key idea behind Newton-Raphson is to use sequential linearization

General form of problem: Find an \mathbf{x} such that

$$\mathbf{f}(\hat{\mathbf{x}}) = 0$$

Newton-Raphson Power Flow



In the Newton-Raphson power flow we use Newton's method to determine the voltage magnitude and angle at each bus in the power system.

We need to solve the power balance equations

$$P_i = \sum_{k=1}^n |V_i| |V_k| (G_{ik} \cos \theta_{ik} + B_{ik} \sin \theta_{ik}) = P_{Gi} - P_{Di}$$

$$Q_i = \sum_{k=1}^n |V_i| |V_k| (G_{ik} \sin \theta_{ik} - B_{ik} \cos \theta_{ik}) = Q_{Gi} - Q_{Di}$$

Power Flow Variables



Assume the slack bus is the first bus (with a fixed voltage angle/magnitude). We then need to determine the voltage angle/magnitude at the other buses.

$$\mathbf{x} = \begin{bmatrix} \theta_2 \\ \vdots \\ \theta_n \\ |V_2| \\ \vdots \\ |V_n| \end{bmatrix} \quad \mathbf{f}(\mathbf{x}) = \begin{bmatrix} P_2(\mathbf{x}) - P_{G2} + P_{D2} \\ \vdots \\ P_n(\mathbf{x}) - P_{Gn} + P_{Dn} \\ Q_2(\mathbf{x}) - Q_{G2} + Q_{D2} \\ \vdots \\ Q_n(\mathbf{x}) - Q_{Gn} + Q_{Dn} \end{bmatrix}$$

N-R Power Flow Solution



The power flow is solved using the same procedure discussed with the general Newton-Raphson:

Set $v = 0$; make an initial guess of \mathbf{x} , $\mathbf{x}^{(v)}$

While $\|\mathbf{f}(\mathbf{x}^{(v)})\| > \varepsilon$ Do

$$\mathbf{x}^{(v+1)} = \mathbf{x}^{(v)} - \mathbf{J}(\mathbf{x}^{(v)})^{-1} \mathbf{f}(\mathbf{x}^{(v)})$$

$$v = v + 1$$

End While

Power Flow Jacobian Matrix



The most difficult part of the algorithm is determining and inverting the n by n Jacobian matrix, $\mathbf{J}(\mathbf{x})$

$$\mathbf{J}(\mathbf{x}) = \begin{bmatrix} \frac{\partial f_1(\mathbf{x})}{\partial x_1} & \frac{\partial f_1(\mathbf{x})}{\partial x_2} & \dots & \frac{\partial f_1(\mathbf{x})}{\partial x_n} \\ \frac{\partial f_2(\mathbf{x})}{\partial x_1} & \frac{\partial f_2(\mathbf{x})}{\partial x_2} & \dots & \frac{\partial f_2(\mathbf{x})}{\partial x_n} \\ \vdots & \ddots & \ddots & \vdots \\ \frac{\partial f_n(\mathbf{x})}{\partial x_1} & \frac{\partial f_n(\mathbf{x})}{\partial x_2} & \dots & \frac{\partial f_n(\mathbf{x})}{\partial x_n} \end{bmatrix}$$

Power Flow Jacobian Matrix, cont'd



Jacobian elements are calculated by differentiating each function, $f_i(\mathbf{x})$, with respect to each variable.

For example, if $f_i(\mathbf{x})$ is the bus i real power equation

$$f_i(x) = \sum_{k=1}^n |V_i| |V_k| (G_{ik} \cos \theta_{ik} + B_{ik} \sin \theta_{ik}) - P_{Gi} + P_{Di}$$


$$\frac{\partial f_i(x)}{\partial \theta_i} = \sum_{\substack{k=1 \\ k \neq i}}^n |V_i| |V_k| (-G_{ik} \sin \theta_{ik} + B_{ik} \cos \theta_{ik})$$

$$\frac{\partial f_i(x)}{\partial \theta_j} = |V_i| |V_j| (G_{ik} \sin \theta_{ik} - B_{ik} \cos \theta_{ik}) \quad (j \neq i)$$

Two Bus Newton-Raphson Example



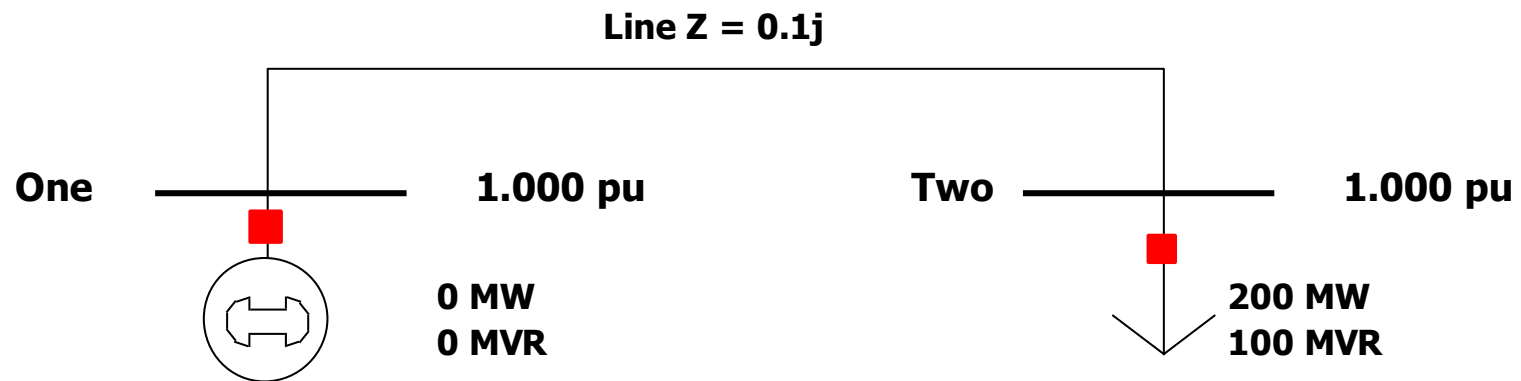- For the two bus power system shown below, use the Newton-Raphson power flow to determine the voltage magnitude and angle at bus two. Assume that bus one is the slack and $S_{Base} = 100 \text{ MVA}$.



$$\mathbf{x} = \begin{bmatrix} \theta_2 \\ |V_2| \end{bmatrix} \quad \mathbf{Y}_{bus} = \begin{bmatrix} -j10 & j10 \\ j10 & -j10 \end{bmatrix}$$

Two Bus Example, cont'd



General power balance equations

$$P_i = \sum_{k=1}^n |V_i||V_k|(G_{ik} \cos \theta_{ik} + B_{ik} \sin \theta_{ik}) = P_{Gi} - P_{Di}$$

$$Q_i = \sum_{k=1}^n |V_i||V_k|(G_{ik} \sin \theta_{ik} - B_{ik} \cos \theta_{ik}) = Q_{Gi} - Q_{Di}$$

Bus two power balance equations

$$|V_2||V_1|(10 \sin \theta_2) + 2.0 = 0$$

$$|V_2||V_1|(-10 \cos \theta_2) + |V_2|^2 (10) + 1.0 = 0$$

Two Bus Example, cont'd



$$P_2(\mathbf{x}) = |V_2|(10\sin\theta_2) + 2.0 = 0$$

$$Q_2(\mathbf{x}) = |V_2|(-10\cos\theta_2) + |V_2|^2(10) + 1.0 = 0$$

Now calculate the power flow Jacobian

$$J(\mathbf{x}) = \begin{bmatrix} \frac{\partial P_2(\mathbf{x})}{\partial \theta_2} & \frac{\partial P_2(\mathbf{x})}{\partial |V|_2} \\ \frac{\partial Q_2(\mathbf{x})}{\partial \theta_2} & \frac{\partial Q_2(\mathbf{x})}{\partial |V|_2} \end{bmatrix}$$
$$= \begin{bmatrix} 10|V_2|\cos\theta_2 & 10\sin\theta_2 \\ 10|V_2|\sin\theta_2 & -10\cos\theta_2 + 20|V_2| \end{bmatrix}$$

Two Bus Example, First Iteration



$$\text{Set } v = 0, \text{ guess } \mathbf{x}^{(0)} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

Calculate

$$\mathbf{f}(\mathbf{x}^{(0)}) = \begin{bmatrix} |V_2|(10\sin\theta_2) + 2.0 \\ |V_2|(-10\cos\theta_2) + |V_2|^2(10) + 1.0 \end{bmatrix} = \begin{bmatrix} 2.0 \\ 1.0 \end{bmatrix}$$

$$\mathbf{J}(\mathbf{x}^{(0)}) = \begin{bmatrix} 10|V_2|\cos\theta_2 & 10\sin\theta_2 \\ 10|V_2|\sin\theta_2 & -10\cos\theta_2 + 20|V_2| \end{bmatrix} = \begin{bmatrix} 10 & 0 \\ 0 & 10 \end{bmatrix}$$

$$\text{Solve } \mathbf{x}^{(1)} = \begin{bmatrix} 0 \\ 1 \end{bmatrix} - \begin{bmatrix} 10 & 0 \\ 0 & 10 \end{bmatrix}^{-1} \begin{bmatrix} 2.0 \\ 1.0 \end{bmatrix} = \begin{bmatrix} -0.2 \\ 0.9 \end{bmatrix}$$

Two Bus Example, Next Iterations



$$\mathbf{f}(\mathbf{x}^{(1)}) = \begin{bmatrix} 0.9(10\sin(-0.2)) + 2.0 \\ 0.9(-10\cos(-0.2)) + 0.9^2 \times 10 + 1.0 \end{bmatrix} = \begin{bmatrix} 0.212 \\ 0.279 \end{bmatrix}$$

$$\mathbf{J}(\mathbf{x}^{(1)}) = \begin{bmatrix} 8.82 & -1.986 \\ -1.788 & 8.199 \end{bmatrix}$$

$$\mathbf{x}^{(2)} = \begin{bmatrix} -0.2 \\ 0.9 \end{bmatrix} - \begin{bmatrix} 8.82 & -1.986 \\ -1.788 & 8.199 \end{bmatrix}^{-1} \begin{bmatrix} 0.212 \\ 0.279 \end{bmatrix} = \begin{bmatrix} -0.233 \\ 0.8586 \end{bmatrix}$$


$$\mathbf{f}(\mathbf{x}^{(2)}) = \begin{bmatrix} 0.0145 \\ 0.0190 \end{bmatrix} \quad \mathbf{x}^{(3)} = \begin{bmatrix} -0.236 \\ 0.8554 \end{bmatrix}$$

$$\mathbf{f}(\mathbf{x}^{(3)}) = \begin{bmatrix} 0.0000906 \\ 0.0001175 \end{bmatrix} \quad \text{Done!} \quad V_2 = 0.8554 \angle -13.52^\circ$$

Two Bus Solved Values



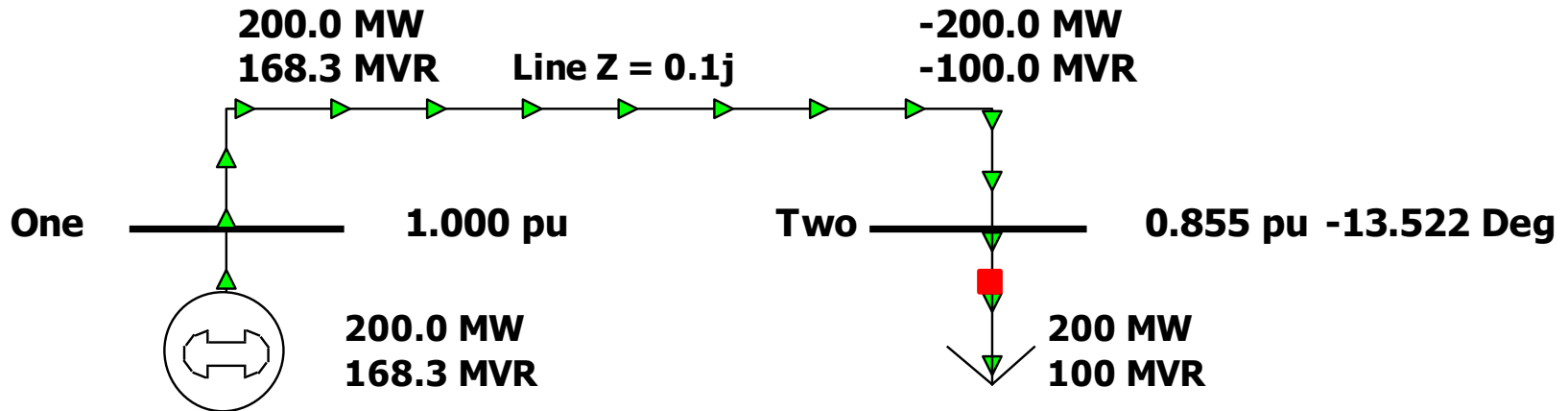- Once the voltage angle and magnitude at bus 2 are known we can calculate all the other system values, such as the line flows and the generator reactive power



PowerWorld Case Name: **Bus2_Intro**

Note, most PowerWorld cases will be available on course website