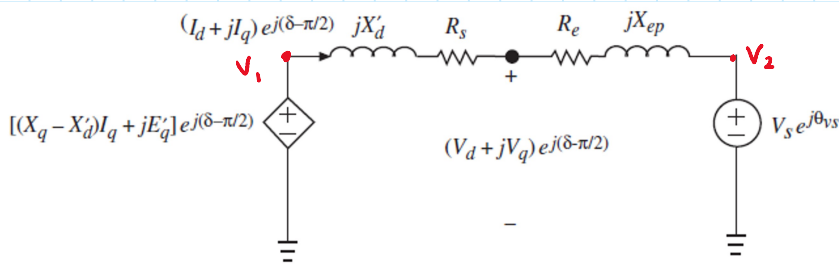


Homework #3, Problem #1

Wednesday, September 29, 2021 1:45 PM

5.2 Given the one-axis dynamic circuit of Figure 5.3, solve for I_d and I_q in terms of the circuit parameters plus δ , E'_q and the source V_s, θ_{vs} .



By Ohm's Law:

$$(I_d + jI_q) e^{j(\delta - \pi/2)} = \frac{V_1 - V_2}{(R_s + jX'_d) + (R_e + jX_{ep})}$$

where: $V_1 = [(X_q - X'_d)I_q + jE'_q] e^{j(\delta - \pi/2)}$

$V_2 = V_s e^{j\theta_{vs}}$

eliminating from both sides ↓

$$\Rightarrow (I_d + jI_q) \cancel{e^{j(\delta - \pi/2)}} = \frac{([(X_q - X'_d)I_q + jE'_q] - V_s e^{j(\theta_{vs} - \delta + \pi/2)}) \cancel{e^{j(\delta - \pi/2)}}}{(R_s + R_e) + j(X'_d + X_{ep})}$$

$$\Rightarrow I_d + jI_q = \frac{[(X_q - X'_d)I_q + jE'_q] - V_s e^{j(\theta_{vs} - \delta + \pi/2)}}{(R_s + R_e) + j(X'_d + X_{ep})} \leftarrow \text{converting to rectangular form}$$

$$= \frac{[(X_q - X'_d)I_q + jE'_q] - (V_s \cos(\theta_{vs} - \delta + \pi/2) + jV_s \sin(\theta_{vs} - \delta + \pi/2))}{(R_s + R_e) + j(X'_d + X_{ep})}$$

$\cos(\theta + \pi/2) = -\sin\theta$ $\sin(\theta + \pi/2) = \cos(\theta)$

$$= \frac{[(X_q - X'_d)I_q + jE'_q] + V_s \sin(\theta_{vs} - \delta) - jV_s \cos(\theta_{vs} - \delta)}{(R_s + R_e) + j(X'_d + X_{ep})}$$

$$= \frac{[(X_q - X'_d)I_q + V_s \sin(\theta_{vs} - \delta)] + j[E'_q - V_s \cos(\theta_{vs} - \delta)]}{(R_s + R_e) + j(X'_d + X_{ep})}$$

↑ Multiply numerator / denominator by the complex conjugate.

$$= \frac{[(X_q - X'_d)I_q + V_s \sin(\theta_{vs} - \delta)] + j[E'_q - V_s \cos(\theta_{vs} - \delta)]}{(R_s + R_e) + j(X'_d + X_{ep})} \times \frac{(R_s + R_e) - j(X'_d + X_{ep})}{(R_s + R_e) - j(X'_d + X_{ep})}$$

For the denominator:

$$\begin{aligned} & [(R_s + R_e) + j(X'_d + X_{ep})] \times [(R_s + R_e) - j(X'_d + X_{ep})] \\ &= (R_s + R_e)^2 + (X'_d + X_{ep})^2 \end{aligned}$$

For the numerator:

$$\begin{aligned} &= [(X_q - X'_d)I_q + V_s \sin(\theta_{vs} - \delta)](R_s + R_e) - \\ & \quad - j[(X_q - X'_d)I_q + V_s \sin(\theta_{vs} - \delta)](X'_d + X_{ep}) + \quad \cdot \text{Green: Real} \\ & \quad + j[E'_q - V_s \cos(\theta_{vs} - \delta)](R_s + R_e) + \quad \cdot \text{Red: Complex} \\ & \quad + [E'_q - V_s \cos(\theta_{vs} - \delta)](X'_d + X_{ep}) \end{aligned}$$

For the real component:

$$I_d = \frac{[(X_q - X'_d)I_q + V_s \sin(\theta_{vs} - \delta)](R_s + R_e) + [E'_q - V_s \cos(\theta_{vs} - \delta)](X'_d + X_{ep})}{(R_s + R_e)^2 + (X'_d + X_{ep})^2}$$

For the imaginary component:

$$I_q = \frac{[E'_q - V_s \cos(\theta_{vs} - \delta)](R_s + R_e) - [(X_q - X'_d)I_q + V_s \sin(\theta_{vs} - \delta)](X'_d + X_{ep})}{(R_s + R_e)^2 + (X'_d + X_{ep})^2}$$

Thus we have two equations with two unknowns. Plugging this into an equation solver, we get:

$$I_q = \frac{(R_s + R_e)[E'_q - V_s \cos(\delta - \theta_{vs})] + (X'_d + X_{ep})V_s \sin(\delta - \theta_{vs})}{(R_s + R_e)^2 + (X'_d + X_{ep})(X_{ep} + X_d)}$$

$$I_q = \frac{(R_s + R_e) [E'_q - V_s \cos(\delta - \theta_{us})] + (X'_d + X_{ep}) V_s \sin(\delta - \theta_{us})}{(R_s + R_e)^2 + (X'_d + X_{ep})(X_{ep} + X_q)}$$

$$I_d = \frac{(X_{ep} + X_q) [E'_q - V_s \cos(\delta - \theta_{us})] - (R_e + R_s) V_s \sin(\delta - \theta_{us})}{(R_s + R_e)^2 + (X'_d + X_{ep})(X_{ep} + X_q)}$$

Homework #3, Problem #2

Wednesday, September 29, 2021 5:48 PM


Given a synchronous generator with a two-axis model:

$$(V_d + jV_q)e^{j(\delta - \pi/2)} = 1 \angle 0 \text{ pu}$$

$$(I_d + jI_q)e^{j(\delta - \pi/2)} = 0.5 \angle 30^\circ \text{ pu}$$

$$R_s = 0 \text{ pu}, X_d = \dots \text{ pu}, X_q = \dots \text{ pu}, X'_d = 0.2 \text{ pu}, X'_q = 0.2 \text{ pu}$$

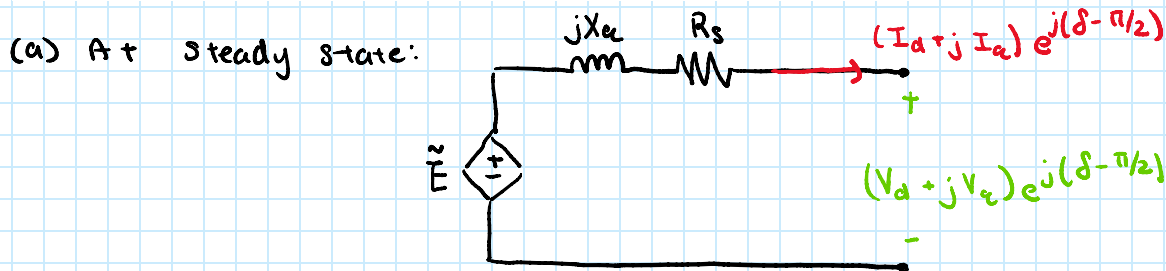- (a) Find the steady-state values of δ , E'_q , E'_d .
- (b) Find the inputs E_{fd} and T_m .
- (c) Find E'^o and δ'^o for the classical model.



$$\Rightarrow |E| \angle \delta = (R_s + jX_s)(I_d + jI_q)e^{j(\delta - \pi/2)} + (V_d + jV_q)e^{j(\delta - \pi/2)}$$

$$= j1.1(0.5 \angle 30^\circ) + (1 \angle 0)$$

$$= j1.1[0.5 \cos(30) + j0.5 \sin(30)] + 1$$

$$= 0.867 \angle 33.043^\circ \text{ pu}$$

$$\Rightarrow \boxed{\delta = 33.043^\circ}$$

$$\Rightarrow \begin{bmatrix} V_d \\ V_q \end{bmatrix} = \begin{bmatrix} \sin \delta & -\cos \delta \\ \cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} V_r \\ V_i \end{bmatrix} = \begin{bmatrix} \sin \delta & -\cos \delta \\ \cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \begin{bmatrix} 0.549 \\ 0.836 \end{bmatrix} \text{ pu}$$

$$\begin{bmatrix} I_d \\ I_q \end{bmatrix} = \begin{bmatrix} \sin \delta & -\cos \delta \\ \cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} I_r \\ I_i \end{bmatrix} = \begin{bmatrix} \sin \delta & -\cos \delta \\ \cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} 0.433 \\ 0.25 \end{bmatrix} = \begin{bmatrix} 0.029 \\ 0.499 \end{bmatrix} \text{ pu}$$


$$\Rightarrow \bar{E}'_q = V_q + R_s I_q + X'_d I_d = 0.449 \text{ pu} \Rightarrow \boxed{\bar{E}'_d = 0.449 \text{ pu}}$$

$$\bar{E}'_d = V_d - R_s I_d - X'_q I_q = 0.841 \text{ pu} \quad \boxed{\bar{E}'_q = 0.841 \text{ pu}}$$

Homework #3, Problem #3

Thursday, September 30, 2021 5:47 PM

From Lecture 8, Slide 46

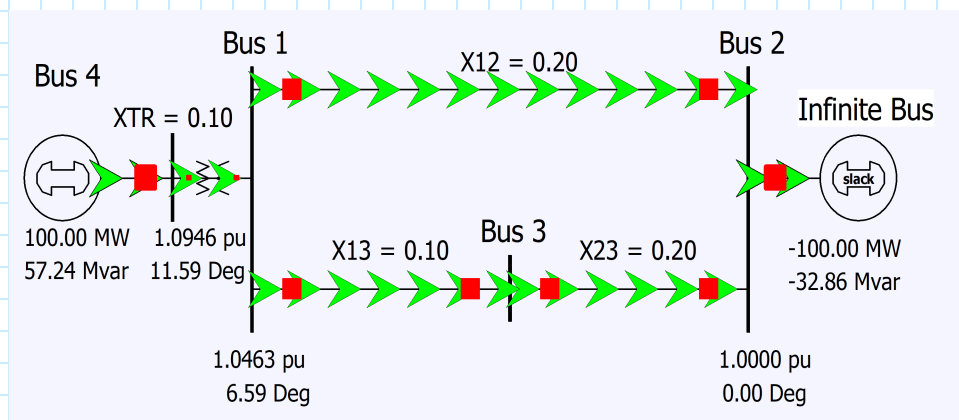

- Generator supplies 1 pu real power at 0.95 pf lagging
- Current is $1\angle 0^\circ$ pu into the bus.

$$\Rightarrow \tilde{I} = 1\angle 0^\circ \text{ pu}$$

$$\tilde{V}_s = (1\angle 0^\circ) + j 0.22 (1\angle 0^\circ)$$

\uparrow voltage at infinite bus
 \uparrow equivalent impedance of line

$$= 1 + j0.22 \text{ pu}$$

$$\Rightarrow |E| \angle \delta = \tilde{V}_s + (R_s + jX_q) \tilde{I}$$

$$= (1 + j0.22) + j 2 (1\angle 0^\circ)$$

$$= 1 + j2.22 = 2.435 \angle 65.751^\circ \text{ pu}$$

$$\Rightarrow \delta = 65.751^\circ$$

$$\Rightarrow \begin{bmatrix} V_d \\ V_q \end{bmatrix} = \begin{bmatrix} \sin \delta & -\cos \delta \\ \cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} V_r \\ V_i \end{bmatrix}$$

$$= \begin{bmatrix} \sin \delta & \cos \delta \\ -\cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} 1 \\ 0.22 \end{bmatrix}$$

$$= \begin{bmatrix} 0.821 \\ 0.611 \end{bmatrix} \text{ pu} \Rightarrow \boxed{\begin{bmatrix} V_d \\ V_q \end{bmatrix} = \begin{bmatrix} 0.821 \\ 0.611 \end{bmatrix} \text{ pu}}$$

$$\Rightarrow \begin{bmatrix} I_d \\ I_q \end{bmatrix} = \begin{bmatrix} \sin \delta & -\cos \delta \\ \cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} I_r \\ I_i \end{bmatrix}$$

$$= \begin{bmatrix} \sin \delta & -\cos \delta \\ \cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

$$= \begin{bmatrix} 0.912 \\ 0.411 \end{bmatrix} \text{ pu} \Rightarrow \boxed{\begin{bmatrix} I_d \\ I_q \end{bmatrix} = \begin{bmatrix} 0.912 \\ 0.411 \end{bmatrix} \text{ pu}}$$

$$\bar{E}'_q = V_q + R_s I_q + X'_d I_d \Rightarrow \boxed{\bar{E}'_q = 0.884 \text{ pu}}$$

$$\bar{E}'_d = V_d - R_s I_d - X'_q I_q \Rightarrow \boxed{\bar{E}'_d = 0.616 \text{ pu}}$$

Homework #3, Problem #4

Wednesday, October 6, 2021 11:15 AM

From the B4 - GENSTAT - SAT system:

$$\begin{array}{llll}
 H = 3.0 & X_d = 2.1 & X_d'' = X_q'' = 0.2 & T_{d0}'' = 0.07 \\
 D = 0 & X_q = 2.0 & X_e = 0.13 & T_{q0}'' = 0.07 \\
 R_a = 0 & X_d' = 0.3 & T_{d0}' = 7.0 & S(1.0) = 0.02 \\
 & & & S(1.2) = 0.1
 \end{array}$$

Given that the power delivered is $2 + j0.2$ pu

$$\begin{aligned}
 S &= V I^* \Rightarrow 2 + j2 = (1 \angle 0) I^* \Rightarrow \tilde{I} = 2 - j2 \text{ pu} \\
 \Rightarrow \tilde{V} &= (1 \angle 0) + j0.22(2 - j2) \\
 &= 1.044 + j0.44 \text{ pu}
 \end{aligned}$$

$$\begin{aligned}
 \Rightarrow |E| \angle \delta &= \tilde{V}_s + (R_s + jX_q) \tilde{I} \\
 &= 4.669 \angle 71.9842^\circ \text{ pu} \\
 \Rightarrow \delta &= 71.9842^\circ
 \end{aligned}$$

$$\begin{aligned}
 \Rightarrow \begin{bmatrix} V_d \\ V_q \end{bmatrix} &= \begin{bmatrix} \sin \delta & -\cos \delta \\ \cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} V_r \\ V_i \end{bmatrix} \\
 &= \begin{bmatrix} \sin \delta & \cos \delta \\ -\cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} 1.044 \\ 0.44 \end{bmatrix} \\
 &= \begin{bmatrix} 0.857 \\ 0.741 \end{bmatrix} \text{ pu} \Rightarrow \begin{bmatrix} V_d \\ V_q \end{bmatrix} = \begin{bmatrix} 0.857 \\ 0.741 \end{bmatrix} \text{ pu}
 \end{aligned}$$

$$\begin{aligned}
 \Rightarrow \begin{bmatrix} I_d \\ I_q \end{bmatrix} &= \begin{bmatrix} \sin \delta & -\cos \delta \\ \cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} I_r \\ I_i \end{bmatrix} \\
 &= \begin{bmatrix} \sin \delta & -\cos \delta \\ \cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} 2 \\ -2 \end{bmatrix}
 \end{aligned}$$

$$= \begin{bmatrix} 1.964 \\ 0.428 \end{bmatrix} \text{ pu} \Rightarrow \boxed{\begin{bmatrix} I_d \\ I_q \end{bmatrix} = \begin{bmatrix} 1.964 \\ 0.428 \end{bmatrix} \text{ pu}}$$

$$\begin{aligned} \Rightarrow E'' &= \tilde{V} + (R_s + jX''') \tilde{I}, \text{ where } X''' = 0.2 \\ &= (1.044 + j0.44) + j0.2(2 - j2) \\ &= 1.084 + j0.84 \text{ pu} \end{aligned}$$

\Rightarrow Assuming $\omega = 1 \text{ pu}$, we get:

$$\begin{aligned} \begin{bmatrix} -\psi_a'' \\ \psi_a'' \end{bmatrix} &= \begin{bmatrix} \sin \delta & -\cos \delta \\ \cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} E_r'' \\ E_i'' \end{bmatrix} \\ &= \begin{bmatrix} \sin \delta & -\cos \delta \\ \cos \delta & \sin \delta \end{bmatrix} \begin{bmatrix} 1.084 \\ 0.84 \end{bmatrix} \\ &= \begin{bmatrix} 0.771 \\ 1.134 \end{bmatrix} \Rightarrow \boxed{\begin{bmatrix} \psi_a'' \\ \psi_d'' \end{bmatrix} = \begin{bmatrix} -0.771 \\ 1.134 \end{bmatrix}} \end{aligned}$$

$$\begin{aligned} \Rightarrow \text{At steady state: } E_q' &= V_q + R_s I_q + X_d' I_d \\ \psi_d' &= E_q' - (X_d' - X_q) I_d \end{aligned}$$

$$\Rightarrow E_q' = 0.741 + 0.3(1.964)$$

$$= 1.3304 \text{ pu}$$

$$\psi_d' = 1.3304 - (0.3 - 0.13)(1.964)$$

$$= 0.997 \text{ pu}$$

$$\Rightarrow \boxed{\begin{aligned} E_q' &= 1.3304 \text{ pu} \\ \psi_d' &= 0.997 \text{ pu} \end{aligned}}$$

- However, when calculating E_{fd} , we need to consider saturation.

Given: $S(1) = 0.02$ $S = B(E_q' - A)^2$

$S(1.2) = 0.1$

$$\Rightarrow B = \frac{S}{(E_q' - A)^2} \Rightarrow B = \frac{S(1)}{(1-A)^2} = \frac{S(1.2)}{(1.2-A)^2}$$


$$\Rightarrow S(1) = \frac{S(1.2)}{(1.2-A)^2} \cdot (1-A)^2$$

$$\Rightarrow (1.2-A)^2 S(1) = (1-A)^2 S(1.2)$$

\Rightarrow Either: $A_1 = 0.838 \Rightarrow B_1 = 0.763$

OR

$A_2 = 1.0618 \Rightarrow B_2 = 5.236$

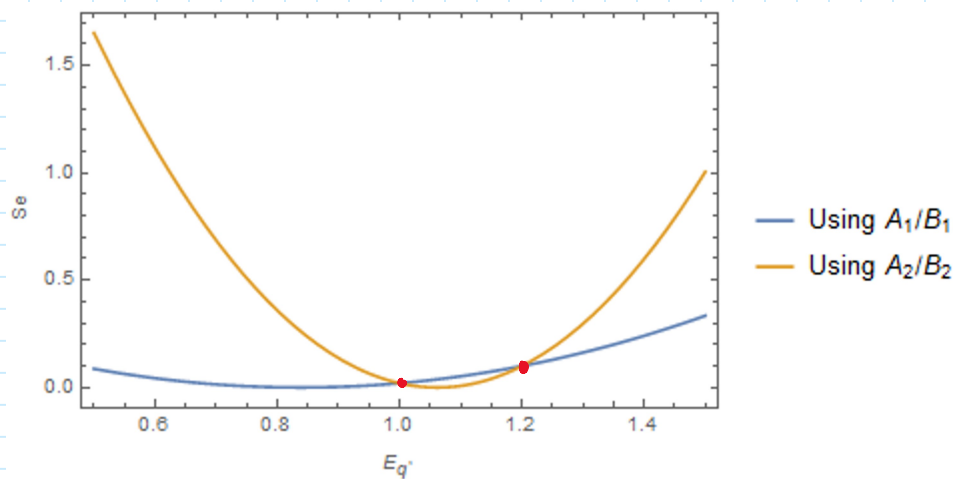

Since we don't want the minimum to be between the marked points, we use $A_1 = 0.838$

$B_1 = 0.763$

$\Rightarrow E_{fd} = E_q' (1 + S(E_q')) + (X_d - X_d') I_d$

$\Rightarrow E_{fd} = 5.112 \text{ pu}$

Homework #3, Problem #5

Wednesday, October 6, 2021 2:23 PM

Parameter	Initial Value	Final Value	Critical Clearing Time	1st Swing Peak	4th Swing Peak	"Damping"	CCT Delta	Damping Delta
Inertia (H)	3	4	0.18	131.977	70.774	0.261011833	0.01	-0.013834096
Damping Factor (D)	0	1	0.17	151.524	73.93	0.242001817	0	-0.032844112
Stator Resistance (Ra)	0	1	0.04	51.765	47.166	-0.763420245	-0.13	-1.038266175
D-Axis Synchronous Reactance (Xd)	2.1	3.1	0.16	142.129	75.071	0.27872908	-0.01	0.003883151
Q-Axis Synchronous Reactance (Xq)	2	3	0.16	145.981	78.391	0.301929274	-0.01	0.027083345
D-Axis Transient Reactance (Xdp)	0.3	1.3	0.1	113.976	55.142	0.092334038	-0.07	-0.182511891
Q-Axis Transient Reactance (Xqp)	0.5	1.5	0.17	145.399	75.743	0.276241142	0	0.001395213
D-Axis Subtransient Reactance (Xdpp)	0.28	0.29	0.17	159.146	80.899	0.288592496	0	0.013746566
Stator Leakage Reactance (Xl)	0.13	0.23	0.17	154.801	80.56	0.297253039	0	0.022407109
Open Circuit D-Axis Transient Time Constant (Tdop)	7	8	0.17	155.975	78.155	0.2714711	0	-0.003374829
Q-Axis Transient Time Constant (Tqop)	0.75	0.85	0.17	157.013	78.079	0.268153835	0	-0.006692094
Open Circuit D-Axis Subtransient Time Constant (Tdopp)	0.073	0.173	0.17	155.444	78.409	0.275217101	0	0.000371172
Q-Axis Subtransient Time Constant (Tqopp)	0.07	0.17	0.17	162.847	86.579	0.329158237	0	0.054312308
Saturation @ 1 flux (S1)	0.05	0.15	0.16	137.917	74.748	0.288316809	-0.01	0.01347088
Saturation @ 1.2 flux (S12)	0.2	0.3	0.17	152.545	73.968	0.239979495	0	-0.034866434
Compensating Resistance (Rcomp)	0	1	0.17	158.36	79.171	0.274845929	0	0
Compensating Reactance (Xcomp)	0	1	0.17	158.36	79.171	0.274845929	0	0

From the above data, we note that the most sensitive parameters are the inertia (H), damping factor (D), stator resistance (Ra), and D-axis transient reactance X_d' .

Thus:

Parameter	CCT Delta	Damping Delta
Inertia (H)	0.01	-0.013834096
Damping Factor (D)	0	-0.032844112
Stator Resistance (Ra)	-0.13	-1.038266175
D-Axis Transient Reactance (Xdp)	-0.07	-0.182511891

Shows how the critical clearing time (CCT) and the damping change as we change the parameters by 1.