

ECEN 667

Power System Stability

Lecture 3: Electromagnetic Transients

Prof. Tom Overbye

Dept. of Electrical and Computer Engineering

Texas A&M University

overbye@tamu.edu



TEXAS A&M
UNIVERSITY

Announcements



- Start reading Chapters 1 and 2 from the book (Chapter 1 is Introduction, Chapter 2 is Electromagnetic Transients)
- EPG Dinner is on September 9 at 5pm; please RSVP using the link that was emailed to all.
- Homework 1 is due on Thursday September 7
- Classic reference paper on EMTP is H.W. Dommel, "Digital Computer Solution of Electromagnetic Transients in Single- and Multiphase Networks," *IEEE Trans. Power App. and Syst.*, vol. PAS-88, pp. 388-399, April 1969

Multistep Methods



- Euler's and Runge-Kutta methods are single step approaches, in that they only use information at $\mathbf{x}(t)$ to determine its value at the next time step
- Multistep methods take advantage of the fact that using we have information about previous time steps $\mathbf{x}(t-\Delta t)$, $\mathbf{x}(t-2\Delta t)$, etc
- These methods can be explicit or implicit (dependent on $\mathbf{x}(t+\Delta t)$ values; we'll just consider the explicit Adams-Bashforth approach

Multistep Motivation



- In determining $\mathbf{x}(t+\Delta t)$ we could use a Taylor series expansion about $\mathbf{x}(t)$

$$\mathbf{x}(t + \Delta t) = \mathbf{x}(t) + \Delta t \dot{\mathbf{x}}(t) + \frac{\Delta t^2}{2} \ddot{\mathbf{x}}(t) + O(\Delta t^3)$$

$$\mathbf{x}(t + \Delta t) = \mathbf{x}(t) + \Delta t \mathbf{f}(t) + \frac{\Delta t^2}{2} \left(\frac{\mathbf{f}(\mathbf{x}(t)) - \mathbf{f}(\mathbf{x}(t - \Delta t))}{\Delta t} + O(\Delta t) \right)$$

$$\mathbf{x}(t + \Delta t) = \mathbf{x}(t) + \Delta t \left(\frac{3}{2} \mathbf{f}(\mathbf{x}(t)) - \frac{1}{2} \mathbf{f}(\mathbf{x}(t - \Delta t)) \right) + O(\Delta t^3)$$

(note Euler's is just the first two terms on the right-hand side)

Adams-Bashforth



- What we derived is the second order Adams-Bashforth approach. Higher order methods are also possible, by approximating subsequent derivatives. Here we also present the third order Adams-Bashforth

Second Order

$$\mathbf{x}(t + \Delta t) = \mathbf{x}(t) + \frac{\Delta t}{2} (3\mathbf{f}(\mathbf{x}(t)) - \mathbf{f}(\mathbf{x}(t - \Delta t))) + O(\Delta t^3)$$

Third Order

$$\mathbf{x}(t + \Delta t) = \mathbf{x}(t) + \frac{\Delta t}{12} (23\mathbf{f}(\mathbf{x}(t)) - 16\mathbf{f}(\mathbf{x}(t - \Delta t)) + 5\mathbf{f}(\mathbf{x}(t - 2\Delta t))) + O(\Delta t^4)$$

Adams-Bashforth Versus Runge-Kutta



- The key Adams-Bashforth advantage is the approach only requires one function evaluation per time step while the RK methods require multiple evaluations
- A key disadvantage is when discontinuities are encountered, such as with limit violations
 - In some simulations limits can be hit often
 - Another method needs to be used until there are sufficient past solutions
- They also have difficulties if variable time steps are used

Numerical Instability

- All explicit methods can suffer from numerical instability if the time step is not correctly chosen for the problem eigenvalues

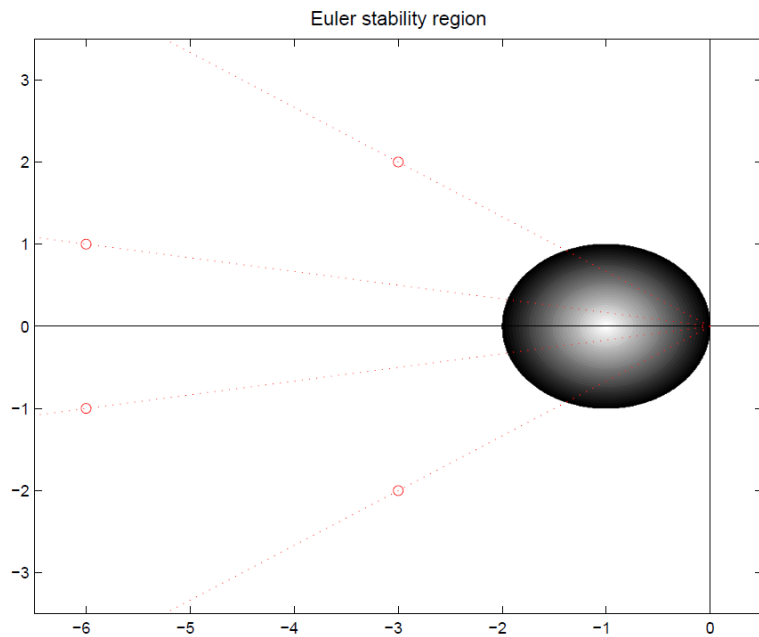


Figure 10.2: The spectrum of A is scaled by h . Stability of the origin is recovered if $h\lambda$ is in the region of absolute stability $|1 + z| < 1$ in the complex plane.

Values are scaled by the time step; the shape for RK2 has similar dimensions but is closer to a square. Key point is to make sure the time step is small enough relative to the eigenvalues.

Stiff Differential Equations



- Stiff differential equations are ones in which the desired solution has components that vary quite rapidly relative to the solution
- Stiffness is associated with solution efficiency: in order to account for these fast dynamics we need to take quite small time steps

$$\dot{x}_1 = x_2$$

$$\dot{x}_2 = -1000x_1 - 1001x_2$$

$$\dot{\mathbf{x}} \rightarrow = \begin{bmatrix} 0 & 1 \\ -1000 & -1000 \end{bmatrix} \mathbf{x}$$

$$x_1(t) = Ae^{-t} + Be^{-1000t}$$

Stiff differential equations are common in power systems, but there are efficient techniques for handling them

Implicit Methods



- Implicit solution methods have the advantage of being numerically stable over the entire left half plane
- Only methods considered here are the Backward Euler and Trapezoidal

$$\dot{\mathbf{x}} = \mathbf{f}(\mathbf{x}(t)) = \mathbf{A}\mathbf{x}(t)$$

Then using backward Euler

$$\mathbf{x}(t + \Delta t) = \mathbf{x}(t) + \Delta t \mathbf{A}(\mathbf{x}(t + \Delta t))$$

$$[I - \Delta t \mathbf{A}] \mathbf{x}(t + \Delta t) = \mathbf{x}(t)$$

$$\mathbf{x}(t + \Delta t) = [I - \Delta t \mathbf{A}]^{-1} \mathbf{x}(t)$$

Initially we'll assume linear equations

Backward Euler Cart Example



- Returning to the cart example

$$\dot{\mathbf{x}} = \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} \mathbf{x}(t)$$

Then using backward Euler with $\Delta t = 0.25$

$$\mathbf{x}(t + \Delta t) = [I - \Delta t \mathbf{A}]^{-1} \mathbf{x}(t) = \begin{bmatrix} 1 & -0.25 \\ 0.25 & 1 \end{bmatrix}^{-1} \mathbf{x}(t)$$

Backward Euler Cart Example



- Results with $\Delta t = 0.25$ and 0.05

time	actual $x_1(t)$	$x_1(t)$ with $\Delta t=0.25$	$x_1(t)$ with $\Delta t=0.05$
0	1	1	1
0.25	0.9689	0.9411	0.9629
0.50	0.8776	0.8304	0.8700
0.75	0.7317	0.6774	0.7185
1.00	0.5403	0.4935	0.5277
2.00	-0.416	-0.298	-0.3944

Note: Just because the method is numerically stable doesn't mean it is error free! RK2 is more accurate than backward Euler.

Trapezoidal Linear Case



- For the trapezoidal with a linear system we have

$$\dot{\mathbf{x}} = \mathbf{f}(\mathbf{x}(t)) = \mathbf{A}\mathbf{x}(t)$$

$$\mathbf{x}(t + \Delta t) = \mathbf{x}(t) + \frac{\Delta t}{2} [\mathbf{A}(\mathbf{x}(t)) + \mathbf{A}(\mathbf{x}(t + \Delta t))]$$

$$\left[I - \frac{\Delta t}{2} \mathbf{A} \right] \mathbf{x}(t + \Delta t) = \left[I + \frac{\Delta t}{2} \mathbf{A} \right] \mathbf{x}(t)$$

$$\mathbf{x}(t + \Delta t) = \left[I - \Delta t \mathbf{A} \right]^{-1} \left[I + \frac{\Delta t}{2} \mathbf{A} \right] \mathbf{x}(t)$$

Trapezoidal Cart Example



- Results with $\Delta t = 0.25$, comparing between backward Euler and trapezoidal

time	actual $x_1(t)$	Backward Euler	Trapezoidal
0	1	1	1
0.25	0.9689	0.9411	0.9692
0.50	0.8776	0.8304	0.8788
0.75	0.7317	0.6774	0.7343
1.00	0.5403	0.4935	0.5446
2.00	-0.416	-0.298	-0.4067

The Best Numerical Integration Approach Depends on the Application



- There is no single best numerical integration method, with all approaches having advantages and disadvantages
- Issues to consider include
 - Speed
 - Accuracy
 - Numerical stability
 - Code complexity; with power system stability this includes the ability to support a wide, and growing list of models
- Explicit methods are commonly used with great success, with numerical instability methods managed through effective engineering
 - An analogy is airplane, which through engineering can be made to effectively fly even though there are conditions in which they can crash

Electromagnetic Transients



- The modeling of very fast power system dynamics (much less than one cycle) is known as electromagnetics transients program (EMTP) analysis
 - Covers issues such as lightning propagation and switching surges; they can also be used with inverter-based controls
- Concept originally developed by Prof. Hermann Dommel for his PhD in the 1960's (now emeritus at Univ. British Columbia)
 - After his PhD work Dr. Dommel worked at BPA where he was joined by Scott Meyer in the early 1970's
 - Alternative Transients Program (ATP) developed in response to commercialization of the BPA code

Power System Time Frames

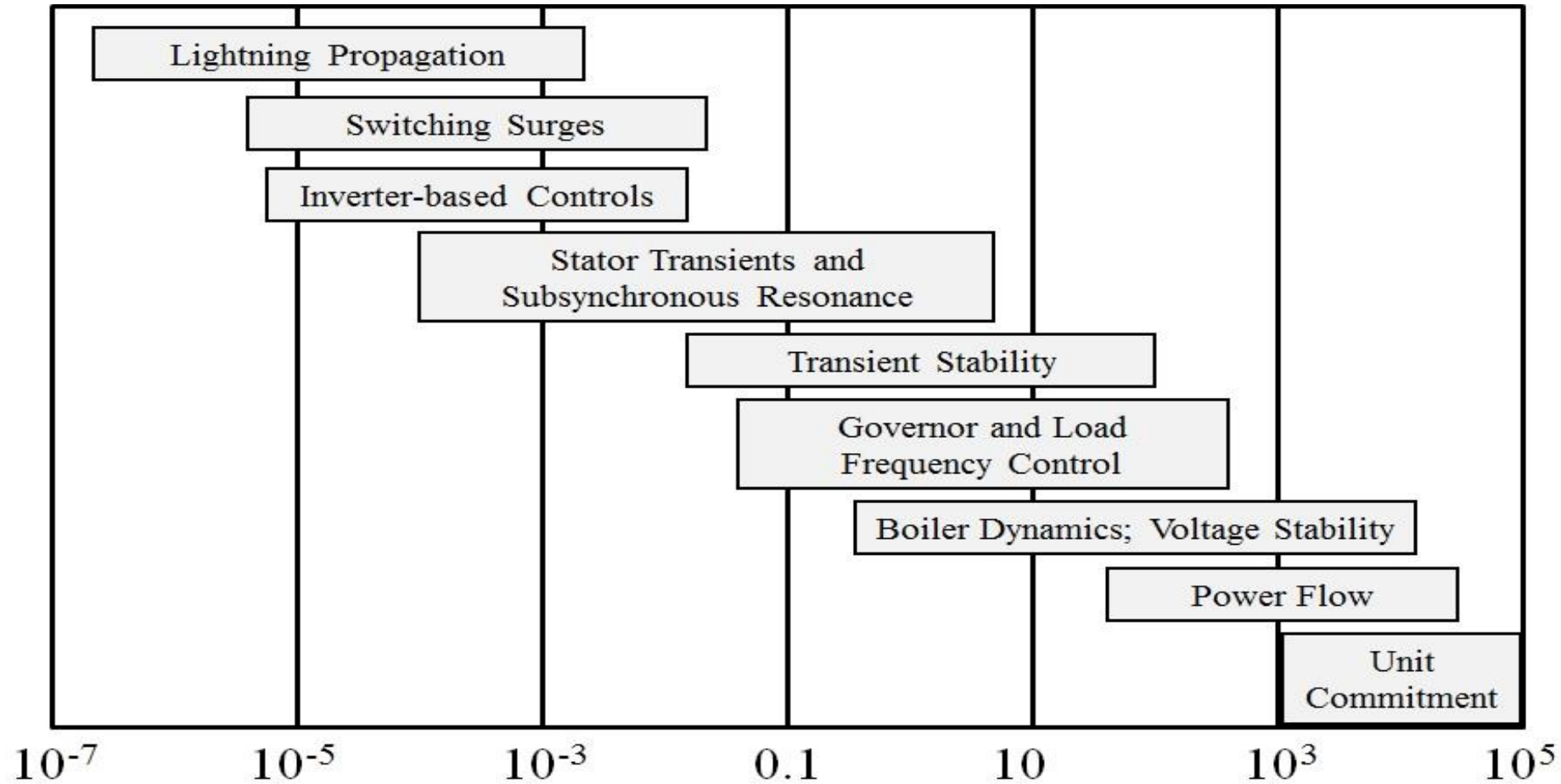


Image source: P.W. Sauer, M.A. Pai, Power System Dynamics and Stability, 1997, Fig 1.2, modified


Transmission Line Modeling




- In power flow and transient stability transmission lines are modeled using a lumped parameter approach
 - Changes in voltages and current in the line are assumed to occur instantaneously
 - Transient stability time steps are usually a few ms (1/4 cycle is common, equal to 4.167ms for 60Hz)
- In EMTP time-frame this is no longer the case; speed of light is 300,000km/sec or 300km/ms or 300m/ μ s
 - Change in voltage and/or current at one end of a transmission cannot instantaneously affect the other end

Need for EMTP

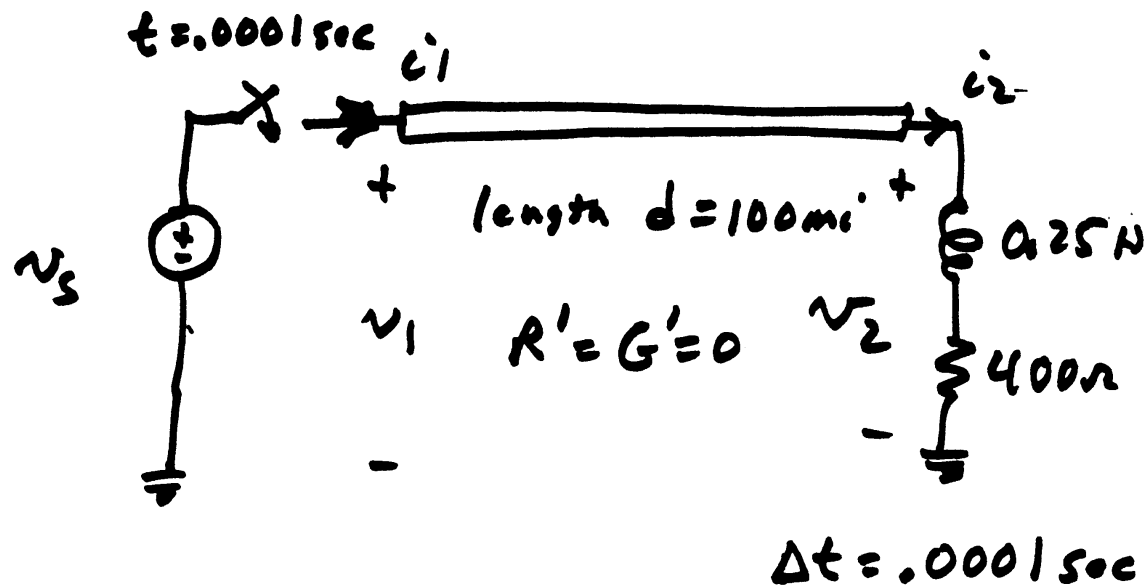
- The change isn't instantaneous because of propagation delays, which are near the speed of light; there also wave reflection issues



Red is the v_s end, green the v_2 end

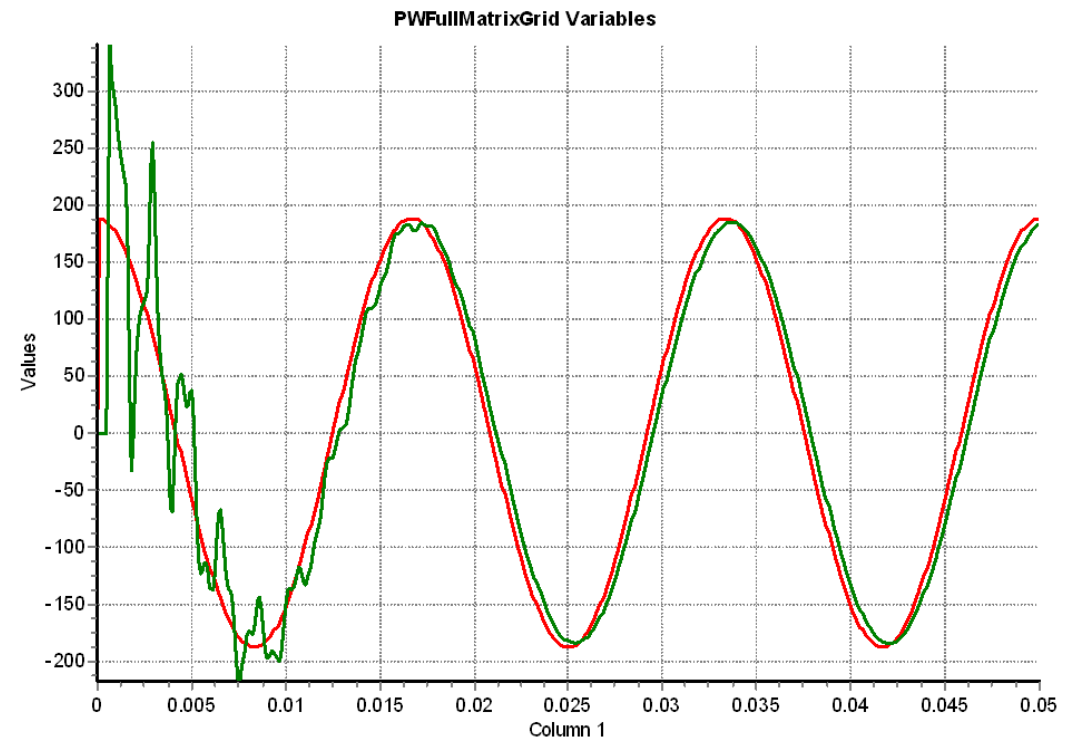

Incremental Transmission Line Modeling

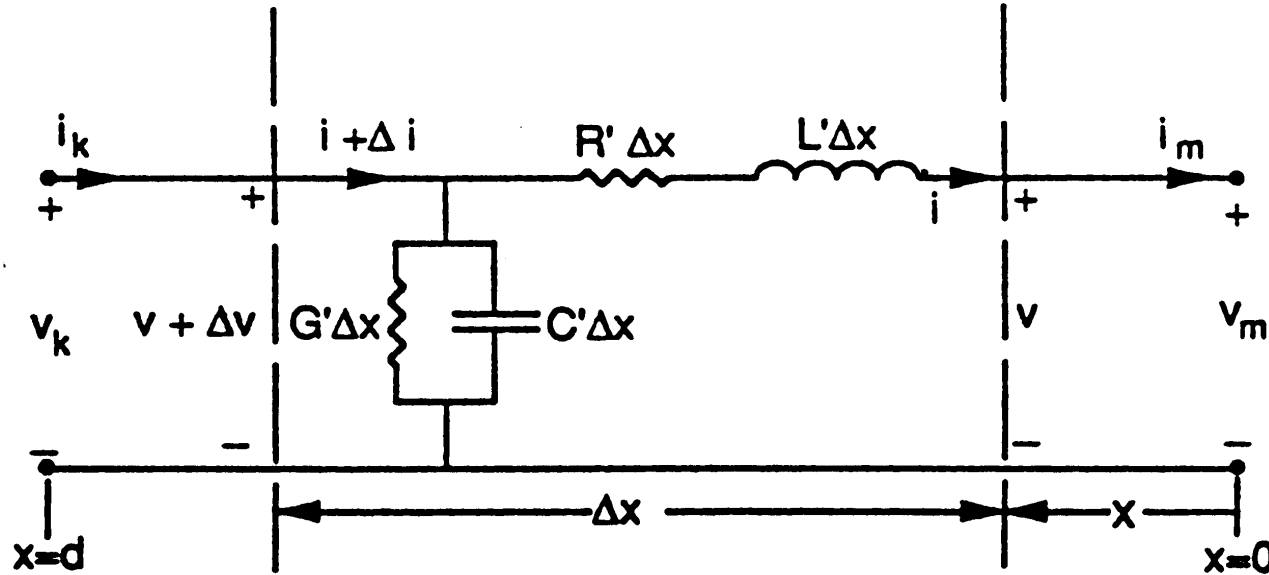


$$\Delta v = R' \Delta x i + L' \Delta x \frac{\partial i}{\partial t}$$

$$\Delta i = G' \Delta x (v + \Delta v) + C' \Delta x \frac{\partial}{\partial t} (v + \Delta v)$$

Define the receiving end as bus m ($x=0$) and the sending end as bus k ($x=d$)

Where We Will End Up

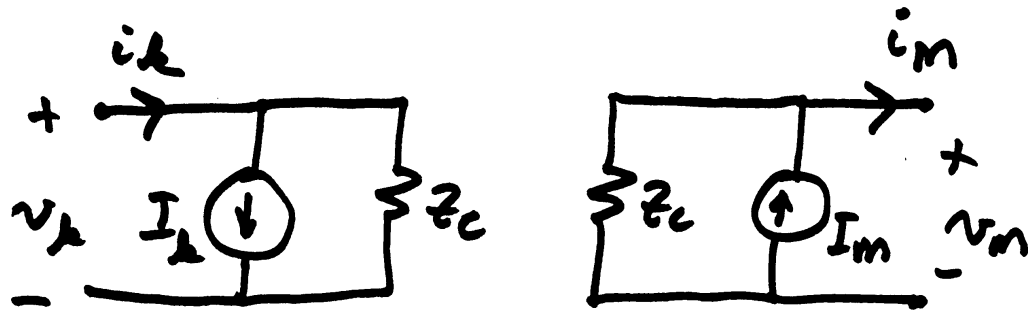- Goal is to come up with model of transmission line suitable for numeric studies on this time frame



Both ends of the line are represented by Norton equivalents

$$I_k = i_m \left(t - \frac{d}{v_p} \right) - \frac{1}{z_c} v_m \left(t - \frac{d}{v_p} \right)$$

Assumption is we don't care about what occurs along the line

$$I_m = i_k \left(t - \frac{d}{v_p} \right) + \frac{1}{z_c} v_k \left(t - \frac{d}{v_p} \right)$$

Incremental Transmission Line Modeling



We are looking to determine $v(x,t)$ and $i(x,t)$

$$\text{Recall } \Delta i = G' \Delta x (v + \Delta v) + C' \Delta x \frac{\partial}{\partial t} (v + \Delta v)$$

$$\text{Substitute } \Delta v = \Delta x \left(R' i + L' \frac{\partial i}{\partial t} \right)$$

Into the equation for Δi and divide both by Δx

$$\frac{\Delta i}{\Delta x} = G' v + G' \left(R' \Delta x i + L' \Delta x \frac{\partial i}{\partial t} \right) + C' \frac{\partial v}{\partial t}$$

$$+ C' \left[R' \Delta x \frac{\partial i}{\partial t} + L' \Delta x \frac{\partial^2 i}{\partial t^2} \right]$$

Incremental Transmission Line Modeling



Taking the limit we get

$$\lim_{\Delta x \rightarrow 0} \frac{\Delta v}{\Delta x} = \frac{\partial v}{\partial x} = R'i + L' \frac{\partial i}{\partial t}$$


$$\lim_{\Delta x \rightarrow 0} \frac{\Delta i}{\Delta x} = \frac{\partial i}{\partial x} = G'v + C' \frac{\partial v}{\partial t}$$

Some authors have a negative sign with these equations; it just depends on the direction of increasing x ; note that the values are function of both x and t

Special Case 1

$C' = G' = 0$ (neglect shunts)
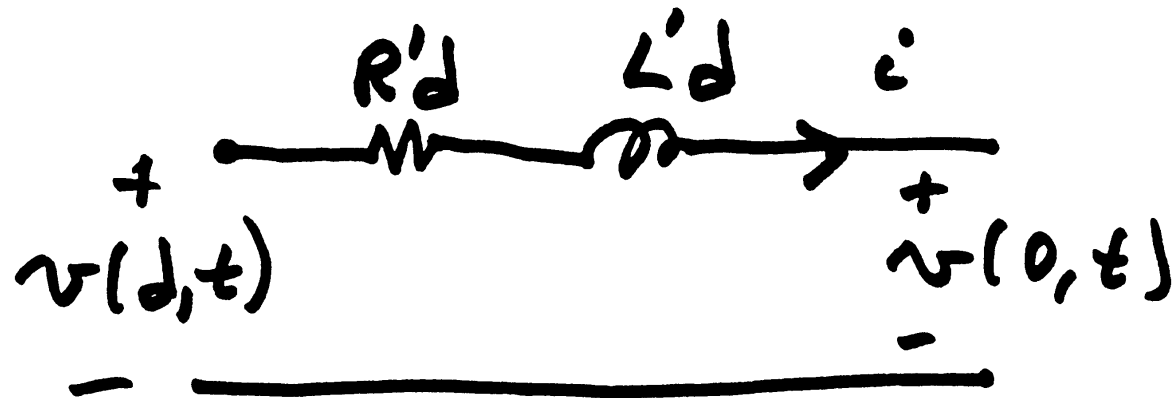
$$v(x,t) = v(0,t) + R'x_i + L'x \frac{di}{dt}$$



This just gives a lumped parameter model, with all electric field effects neglected

Special Case 2: Wave Equation



The lossless line ($R'=0$, $G'=0$), which gives

$$\frac{\partial v}{\partial x} = L' \frac{\partial i}{\partial t}, \quad \frac{\partial i}{\partial x} = C' \frac{\partial v}{\partial t}$$

This is the wave equation with a general solution of

$$i(x, t) = -f_1(x - v_p t) - f_2(x + v_p t)$$

$$v(x, t) = z_c f_1(x - v_p t) - z_c f_2(x + v_p t)$$

$$z_c = \sqrt{L' / C'}, \quad v_p = \frac{1}{\sqrt{L' C'}}$$

Z_c is the characteristic impedance and v_p is the velocity of propagation

Special Case 2: Wave Equation



- This can be thought of as two waves, one traveling in the positive x direction with velocity v_p , and one in the opposite direction
- The values of f_1 and f_2 depend upon the boundary (terminal) conditions

$$i(x,t) = -f_1(x - v_p t) - f_2(x + v_p t)$$

$$v(x,t) = z_c f_1(x - v_p t) - z_c f_2(x + v_p t)$$

$$z_c = \sqrt{L' / C'} , \quad v_p = \frac{1}{\sqrt{L' C'}}$$

Boundaries are receiving end with $x=0$ and the sending end with $x=d$

Calculating v_p



- To calculate v_p for a line in air we go back to the definition of L' and C'

$$L' = \frac{\mu_0}{2\pi} \ln\left(\frac{D}{r'}\right), \quad C' = \frac{2\pi\epsilon_0}{\ln D/r}$$

$$v_p = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{\mu_0\epsilon_0 \frac{\ln D/r'}{\ln D/r}}} = c \frac{1}{\sqrt{\frac{\ln D/r'}{\ln D/r}}}$$

With $r'=0.78r$ this is very close to the speed of light

Important Insight



- The amount of time for the wave to go between the terminals is $d/v_p = \tau$ seconds
 - To an observer traveling along the line with the wave, $x+v_pt$, will appear constant
- What appears at one end of the line impacts the other end τ seconds later

$$i(x,t) = -f_1(x - v_p t) - f_2(x + v_p t)$$

$$v(x,t) = z_c f_1(x - v_p t) - z_c f_2(x + v_p t)$$

$$v(x,t) + z_c i(x,t) = -2z_c f_2(x + v_p t)$$

Both sides of the bottom equation are constant when $x+v_pt$ is constant

Determining the Constants



- If just the terminal characteristics are desired, then an approach known as Bergeron's method can be used.
- Knowing the values at the receiving end m ($x=0$) we get

$$i(x,t) = -f_1(x - v_p t) - f_2(x + v_p t)$$

$$v(x,t) = z_c f_1(x - v_p t) - z_c f_2(x + v_p t)$$

$$i_m(t) = i(0,t) = -f_1(-v_p t) - f_2(v_p t)$$

$$v_m(t) = z_c f_1(-v_p t) - z_c f_2(v_p t)$$

This can be used to eliminate f_1

Determining the Constants



- Eliminating f_1 we get

$$v_m(t) = z_c f_1(-v_p t) - z_c f_2(v_p t)$$

$$f_1(-v_p t) = \frac{v_m(t)}{z_c} + f_2(v_p t)$$

$$i_m(t) = -\frac{v_m}{z_c} - 2f_2(v_p t)$$

Solve for f_1 and replace it in the equation from the previous slide

Determining the Constants



- To solve for f_2 we need to look at what is going on at the sending end (i.e., k at which $x=d$) $\tau = d/v_p$ seconds in the past

$$i_k \left(t - \frac{d}{v_p} \right) = -f_1 \left(d - v_p \left(t - \frac{d}{v_p} \right) \right) - f_2 \left(d + v_p \left(t - \frac{d}{v_p} \right) \right)$$

$$i_k \left(t - \frac{d}{v_p} \right) = -f_1 (2d - v_p t) - f_2 (v_p t)$$

$$v_k \left(t - \frac{d}{v_p} \right) = z_c f_1 (2d - v_p t) - z_c f_2 (v_p t)$$

Determining the Constants



- Dividing v_k by z_c , and then adding it with i_k gives

$$i_k \left(t - \frac{d}{v_p} \right) + \frac{v_k}{z_c} \left(t - \frac{d}{v_p} \right) = -2f_2(v_p t)$$

- Then substituting for f_2 in i_m gives


$$i_m(t) = -\frac{v_m(t)}{z_c} + i_k \left(t - \frac{d}{v_p} \right) + \frac{1}{z_c} v_k \left(t - \frac{d}{v_p} \right)$$

Hence $i_m(t)$ depends on current conditions at m and past conditions at k

Equivalent Circuit Representation

- The receiving end can be represented in circuit form as

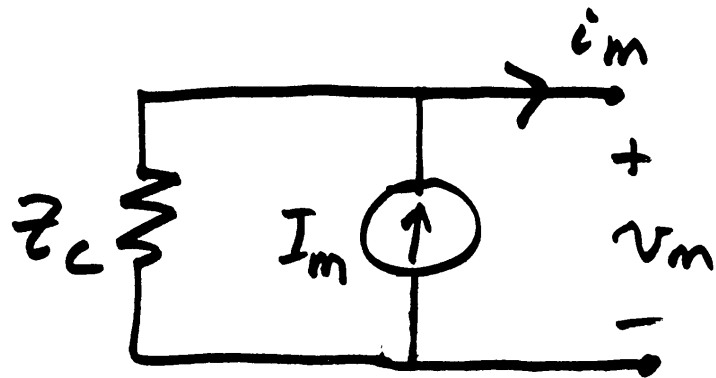
$$i_m(t) = -\frac{v_m(t)}{z_c} + i_k\left(t - \frac{d}{v_p}\right) + \frac{1}{z_c} v_k\left(t - \frac{d}{v_p}\right) \longrightarrow I_m$$



Since $\tau = d/v_p$, I_m just depends on the voltage and current at the other end of the line from τ seconds in the past. Since these are known values, it looks like a time-varying current source.

Repeating for the Sending End

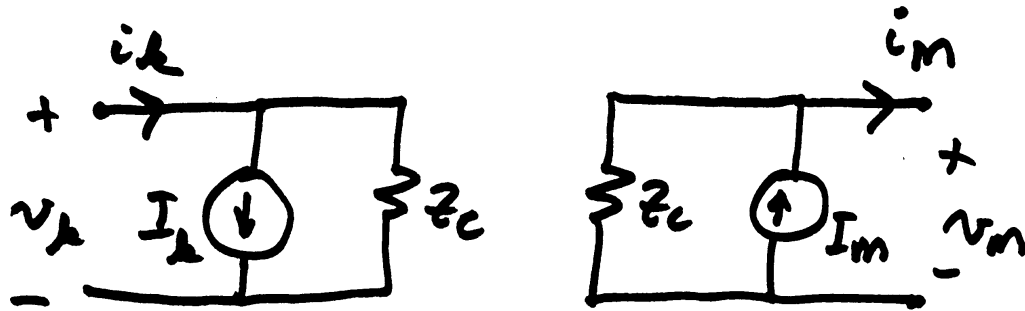- The sending end has a similar representation




Both ends of the line are represented by Norton equivalents

$$I_k = i_m \left(t - \frac{d}{v_p} \right) - \frac{1}{z_c} v_m \left(t - \frac{d}{v_p} \right)$$

$$I_m = i_k \left(t - \frac{d}{v_p} \right) + \frac{1}{z_c} v_k \left(t - \frac{d}{v_p} \right)$$

Lumped Parameter Model

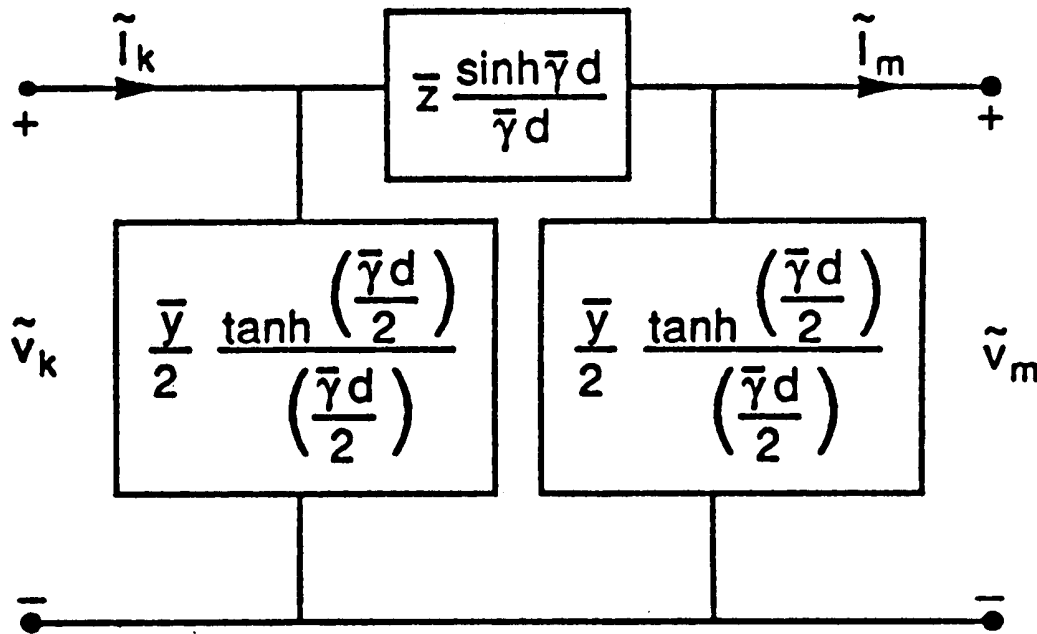- In the special case of constant frequency, book shows the derivation of the common lumped parameter model



This is used in power flow and transient stability; in EMTP the frequency is not constant

Including Line Resistance



- An approach for adding line resistance, while keeping the simplicity of the lossless line model, is to just to place $\frac{1}{2}$ of the resistance at each end of the line
 - Another, more accurate approach, is to place $\frac{1}{4}$ at each end, and $\frac{1}{2}$ in the middle
- Standalone resistance, such as modeling the resistance of a switch, is just represented as an algebraic equation

$$i_{k,m} = \frac{I}{R} (v_k - v_m)$$

Numerical Integration with Trapezoidal Method



- Numerical integration is often done using the trapezoidal method discussed last time
 - Here we show how it can be applied to inductors and capacitors
- For a general function the trapezoidal approach is

$$\dot{\mathbf{x}} = \mathbf{f}(\mathbf{x}(t))$$

$$\mathbf{x}(t + \Delta t) = \mathbf{x}(t) + \frac{\Delta t}{2} [f(\mathbf{x}(t)) + f(\mathbf{x}(t + \Delta t))]$$

- Trapezoidal integration introduces error on the order of Δt^3 , but it is numerically stable

Trapezoidal Applied to Inductor with Resistance



- For a lossless inductor,

$$v = L \frac{di}{dt} \rightarrow \frac{di}{dt} = \frac{v}{L} \quad i(0) = i^0$$

This is a linear equation

$$i(t + \Delta t) = i(t) + \frac{\Delta t}{2L} (v(t) + v(t + \Delta t))$$

- This can be represented as a Norton equivalent with current into the equivalent defined as positive (the last two terms are the current source)

$$i(t + \Delta t) = \frac{v(t + \Delta t)}{2L/\Delta t} + i(t) + \frac{v(t)}{2L/\Delta t}$$


Trapezoidal Applied to Inductor with Resistance



- For an inductor in series with a resistance we have

$$v = iR + L \frac{di}{dt}$$
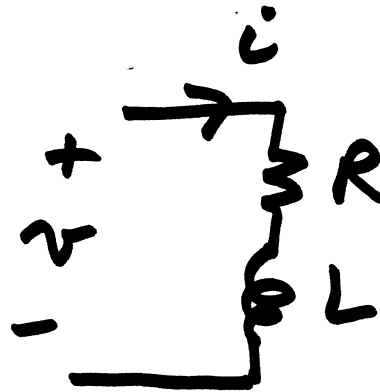
$$\frac{di}{dt} = -\frac{R}{L}i + \frac{1}{L}v \quad i(0) = i^0$$




Trapezoidal Applied to Inductor with Resistance




$$i(t_i + \Delta t) \approx i(t_i) + \frac{\Delta t}{2} \left[-\frac{R}{L} i(t_i) + \frac{1}{L} v(t_i) - \frac{R}{L} i(t_i + \Delta t) + \frac{1}{L} v(t_i + \Delta t) \right]$$

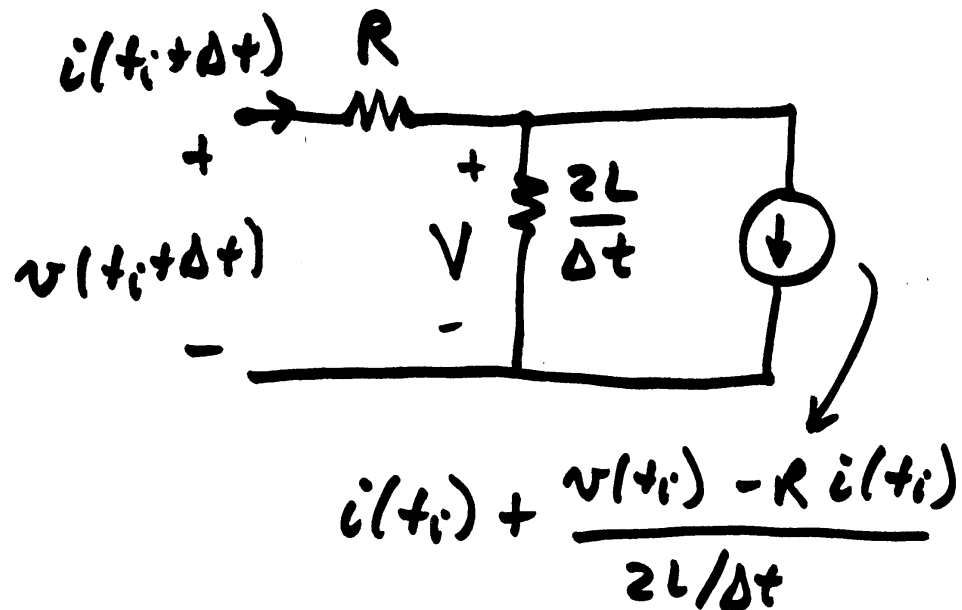This also becomes a Norton equivalent. A similar expression will be developed for capacitors.



RL Example

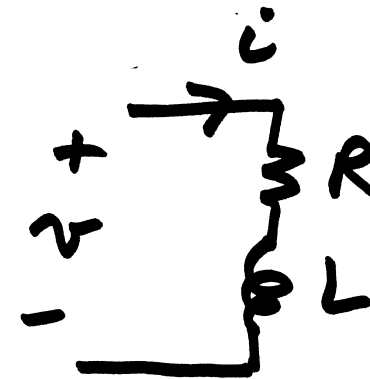- Assume a series RL circuit with an open switch with $R = 200\Omega$ and $L = 0.3\text{H}$, connected to a voltage source with $v = 133,000\sqrt{2}\cos(2\pi 60t)$
- Assume the switch is closed at $t=0$
- The exact solution is



$$i = -712.4e^{-667t} + 578.8\sqrt{2}\cos(2\pi 60t - 29.5^\circ)$$

$$v = iR + L\frac{di}{dt}$$

$$\frac{di}{dt} = -\frac{R}{L}i + \frac{1}{L}v \quad i(0) = i^0$$

$R/L=667$, so the dc offset decays relatively quickly

RL Example Trapezoidal Solution




$$\frac{2L}{\Delta t} = \frac{2 * 0.3}{0.0001} = 6000$$

$$\Delta t = 0.0001 \text{ sec}$$

$$t = 0 \quad i(0) = 0$$

$$t = 0.0001$$
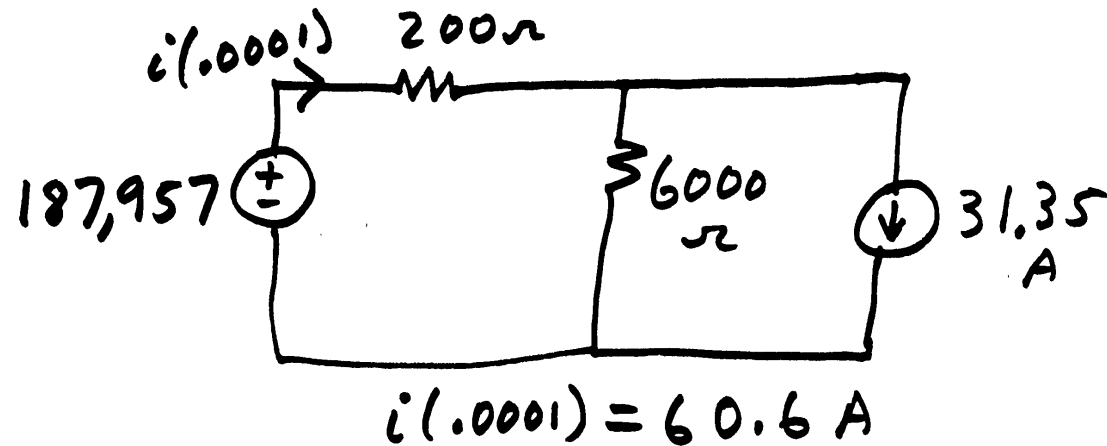
$$i(0) + \frac{v(0) - Ri(0)}{6000} = 31.35 \text{ A}$$



Numeric solution:
$$i(0.0001) = \frac{187,957}{6200} + \frac{31.35 \times 6000}{6200} = 60.65 \text{ A}$$

Exact solution:
$$i(0.0001) = -712.4e^{-0.0677} + 578.8\sqrt{2} \cos\left(2\pi 60 \times .0001 - 29.5 \frac{\pi}{180}\right)$$

$$= -666.4 + 727.0 = 60.6 \text{ A}$$

RL Example Trapezoidal Solution




$$t = 0.0002$$

Solving for $i(0.0002)$


$$i(0.0002) = 117.3A$$

Compare to the exact solution


$$i(0.0002) = 117.3A$$

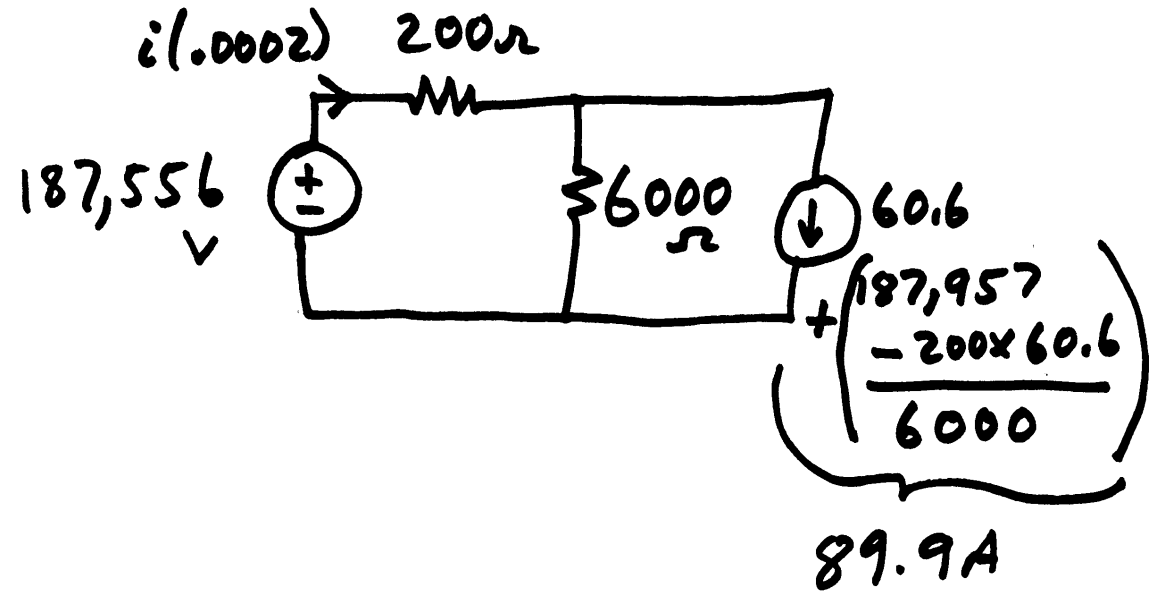

Full Solution Over Three Cycles

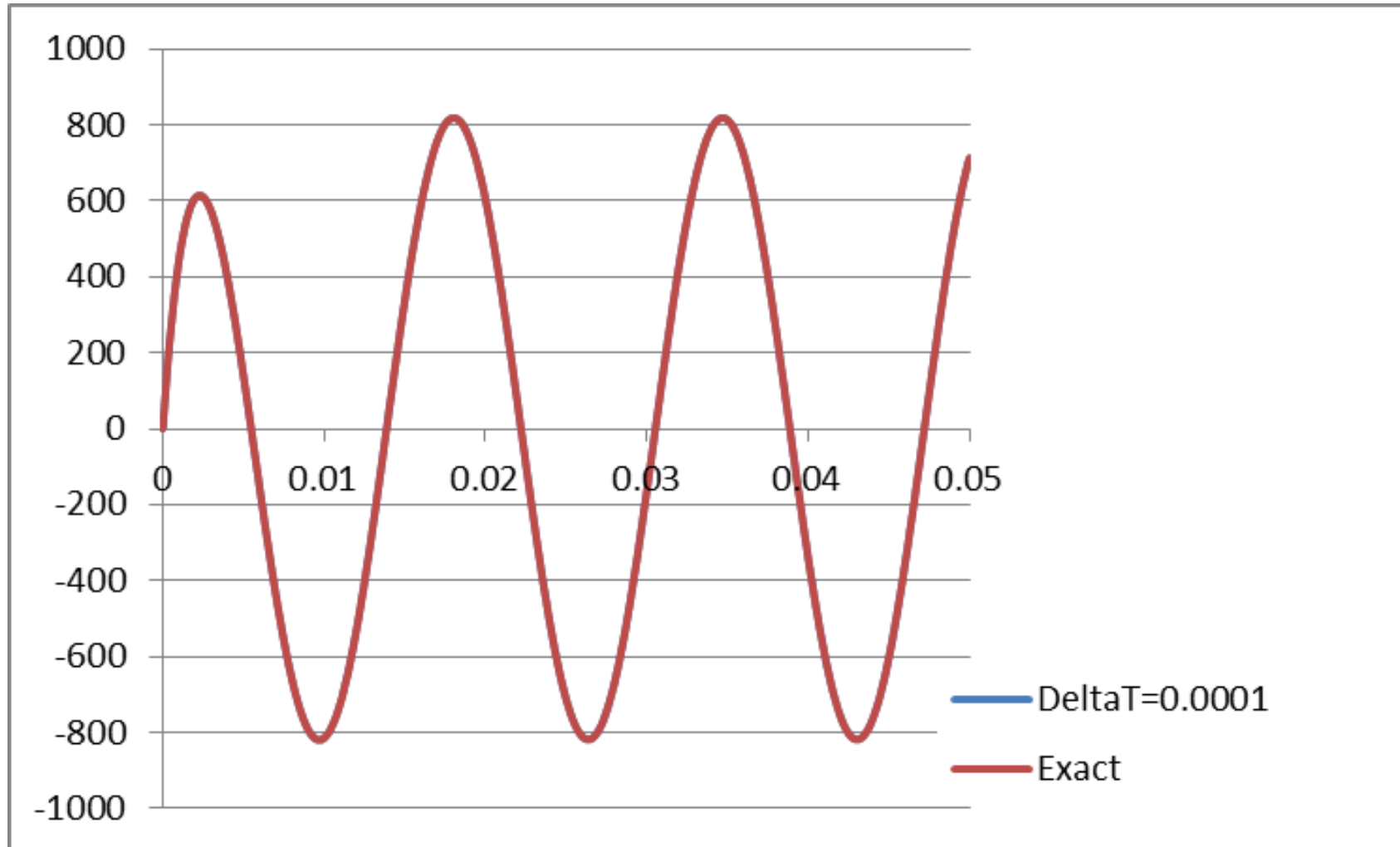

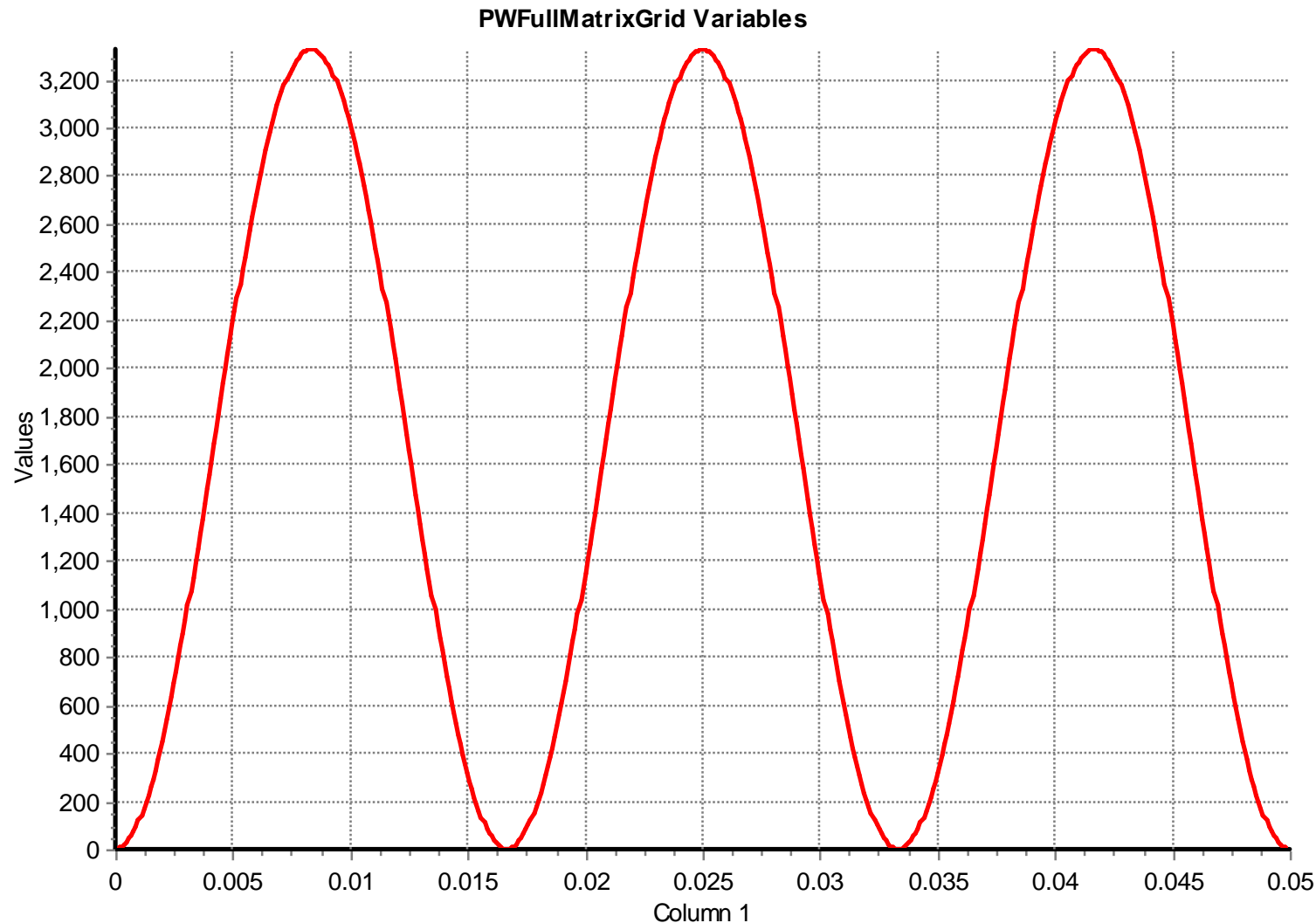A Favorite Problem: R=0 Case, with $v(t) = \text{Sin}(2 \cdot \text{pi} \cdot 60)$



Note that the current is never negative!

Lumped Capacitance Model



- The trapezoidal approach can also be applied to model lumped capacitors

$$i(t) = C \frac{dv(t)}{dt}$$

- Integrating over a time step gives

$$v(t + \Delta t) = v(t) + \frac{1}{C} \int_t^{t+\Delta t} i(t)$$

- Which can be approximated by the trapezoidal as


$$v(t + \Delta t) = v(t) + \frac{\Delta t}{2C} (i(t + \Delta t) + i(t))$$

Lumped Capacitance Model

$$v(t + \Delta t) = v(t) + \frac{\Delta t}{2C} (i(t + \Delta t) + i(t))$$

$$i(t + \Delta t) = \frac{v(t + \Delta t)}{\Delta t/2C} - \frac{v(t)}{\Delta t/2C} - i(t)$$

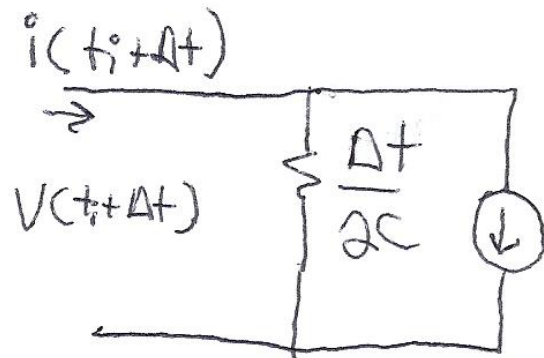
- Hence we can derive a circuit model similar to what was done for the inductor



$$-\frac{v(t)}{\Delta t/2C} - i(t)$$

This is a current source that depends on the past values

Example 2.1: Line Closing

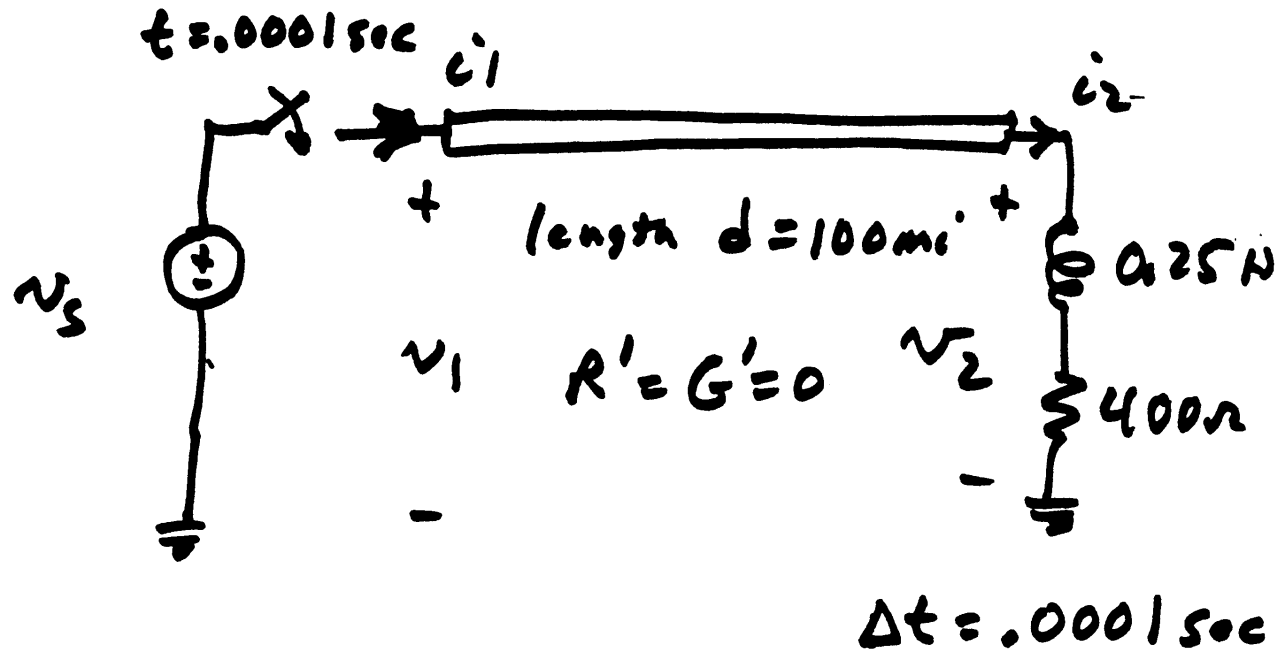

Switch is closed at time $t = 0.0001 \text{ sec}$

$$L' = 1.5 \times 10^{-3} \text{ H / mi}$$

$$C' = 0.02 \times 10^{-6} \text{ F / mi}$$

Example 2.1: Line Closing



Initial conditions: $i_1 = i_2 = v_1 = v_2 = 0$

for $t < 0.0001$ sec

$$z_c = \sqrt{\frac{L'}{C'}} = 274\Omega \quad v_p = \frac{1}{\sqrt{L'C'}} = 182,574 \text{ mi / sec}$$

$$\frac{d}{v_p} = 0.00055 \text{ sec}$$

$$\frac{2L}{\Delta t} = 5000\Omega$$

Because of finite propagation speed, the receiving end of the line will not respond to energizing the sending end for at least 0.00055 seconds.

Example 2.1: Line Closing

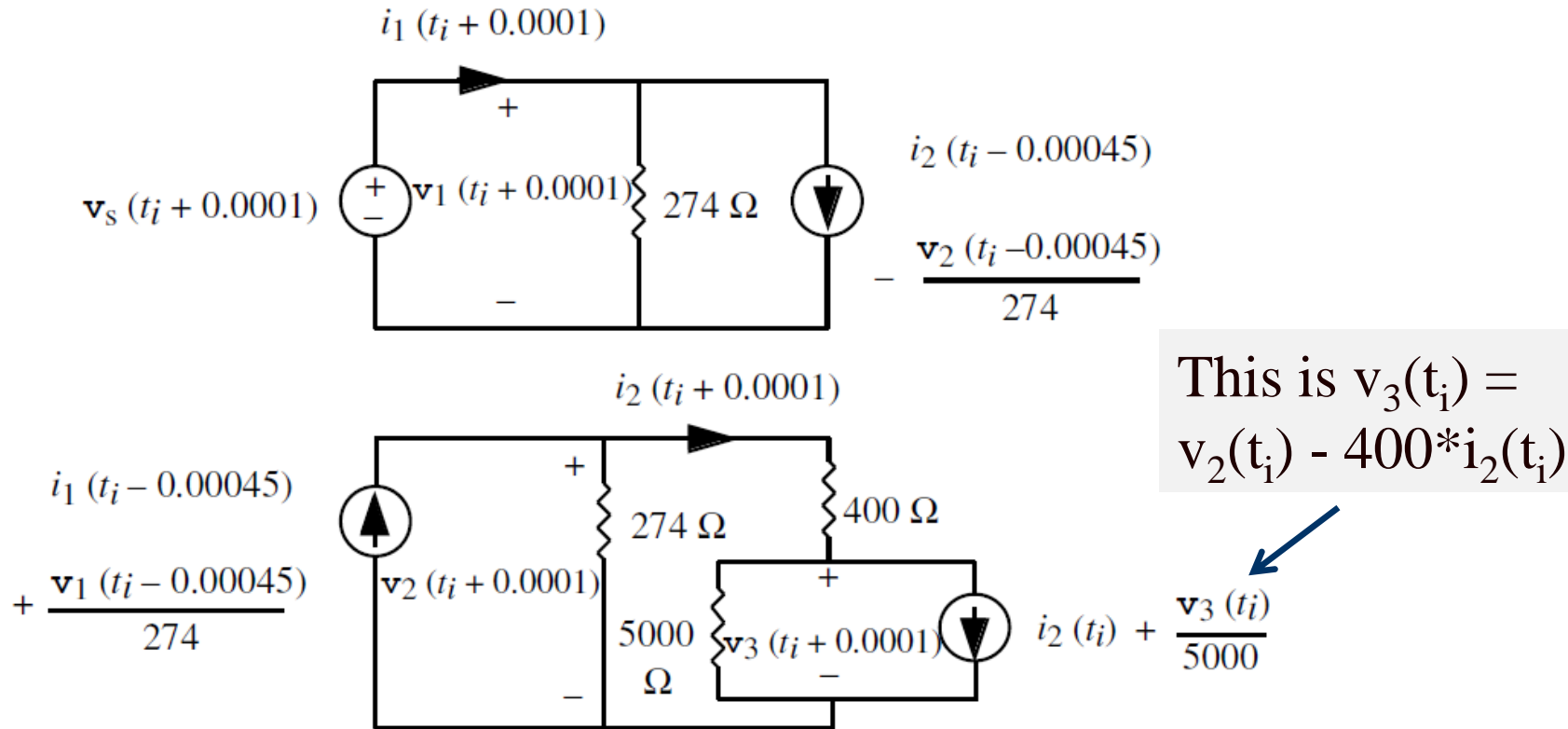


Figure 2.8: Single line and R-L load circuit at $t = t_i + 0.0001$

Note we have two separate circuits, coupled together only by past values.

Example 2.1: $t=0.0001$



Need: $i_1(-0.00045)$, $v_1(-0.00045)$, $i_2(-0.00045)$,
 $v_2(-0.00045)$, $i_2(0)$, $v_3(0)$, $v_s(0.0001)$


$$i_1(-0.00045) = 0 \quad i_2(0) = 0$$

$$v_1(-0.00045) = 0 \quad v_3(0) = 0$$


$$i_2(-0.00045) = 0 \quad v_2(-0.00045) = 0$$

$$v_s(0.0001) = 230,000 \sqrt{\frac{2}{3}} \cos(2\pi 60 \times 0.0001) = 187,661 \text{ V}$$

Example 2.1: $t=0.0001$

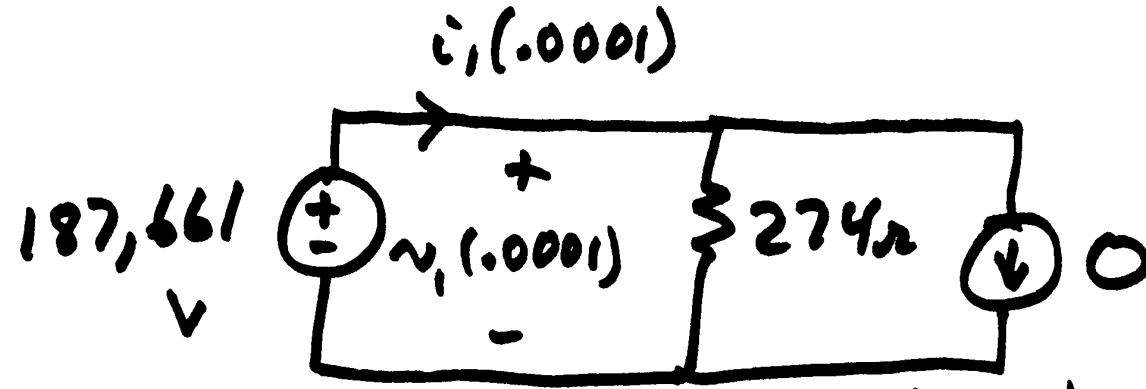

Sending End

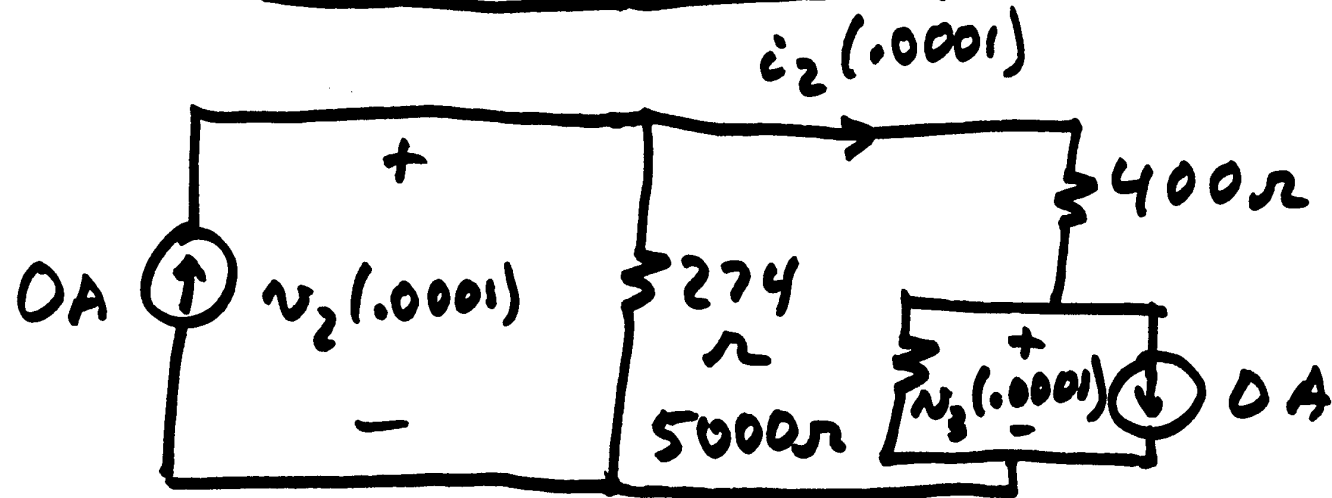

Receiving End

Example 2.1: $t=0.0001$



$$i_1(0.0001) = 685A$$

$$v_1(0.0001) = 187,661V \longrightarrow$$

Instantaneously changed
from zero at $t = 0.0001$ sec.

$$i_2(0.0001) = 0$$

$$v_2(0.0001) = 0$$

$$v_3(0.0001) = 0$$

Example 2.1: $t=0.0002$



Need:

$$i_1(-0.00035) = 0$$

$$v_1(-0.00035) = 0$$

$$i_2(-0.00035) = 0$$

$$v_2(-0.00035) = 0$$

$$i_2(0.0001) = 0$$

$$v_3(0.0001) = 0$$

$$v_s(0.0002) = 187,261V$$

$$i_1(0.0002) = 683A$$

$$v_1(0.0002) = 187,261V$$

$$i_2(0.0002) = 0.$$

$$v_2(0.0002) = 0.$$

$$v_3(0.0002) = 0.$$

Circuit is essentially the same

Wave is traveling down the line

Example 2.1: $t=0.0002$ to 0.006



$$\frac{d}{v_p} = 0.00055 \quad \Delta t = 0.0001$$

$$t_i = 0$$

$$t = 0.0001 \leftarrow \text{switch closed}$$

$$t_i = 0.0001$$

$$t = 0.0002$$

$$= 0.0002$$

$$= 0.0003$$

$$= 0.0003$$

$$= 0.0004$$

$$= 0.0004$$

$$= 0.0005$$

$$= 0.0005$$

$$= 0.0006 \leftarrow \text{With interpolation receiving end will see wave}$$

$$= 0.0006$$

$$= 0.0007 \leftarrow$$

Example 2.1: $t=0.0007$



Need: $i_1(.00015)$

$$i_1(.0001) = 685A$$


$v_1(.00015), v_2(.00015)$

$$i_1(.0002) = 683A$$

$i_2(.0006), v_3(.0006), v_s(.0007)$


(linear interpolation)

$$i_1(.00015) \approx i_1(.0001) + \frac{.00015 - .0001}{.0002 - .0001} \times (i_1(.0002) - i_1(.0001))$$

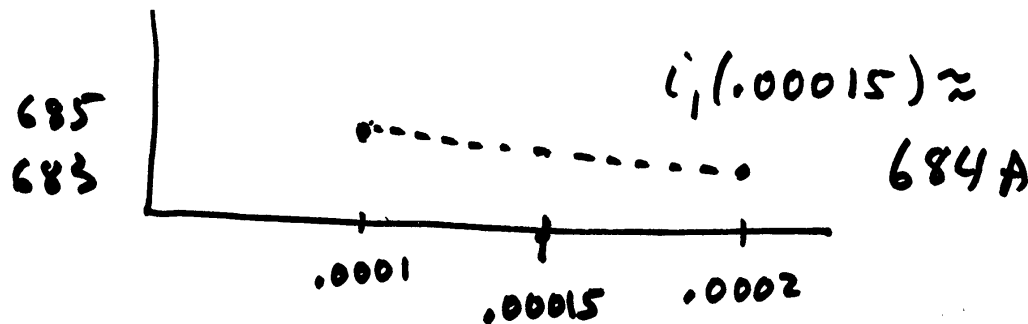

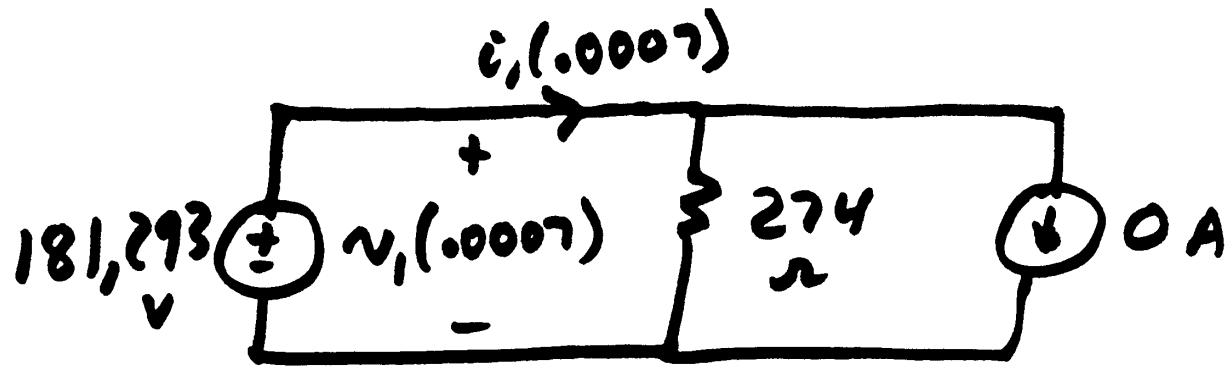Example 2.1: $t=0.0007$

For $t_i = .0006$ ($t = .0007$ sec) at the sending end



This current source will stay zero until we get a response from the receiving end, at about 2τ seconds


$$i_1(.0007) = 662A$$

$$v_1(.0007) = 181,293V$$

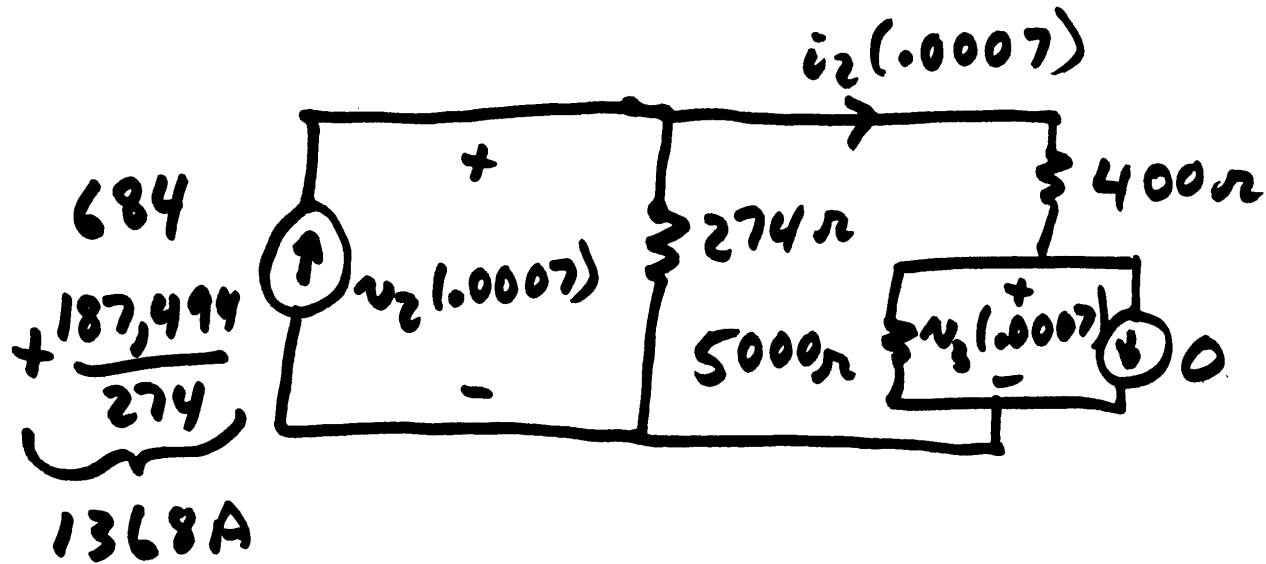Example 2.1: $t=0.0007$




For $t_i = .0006$ ($t = .0007$ sec) at the receiving end



$$v_2(.0007) = 356,731V$$


$$i_2(.0007) = 66A$$

Example 2.1: First Three Cycles

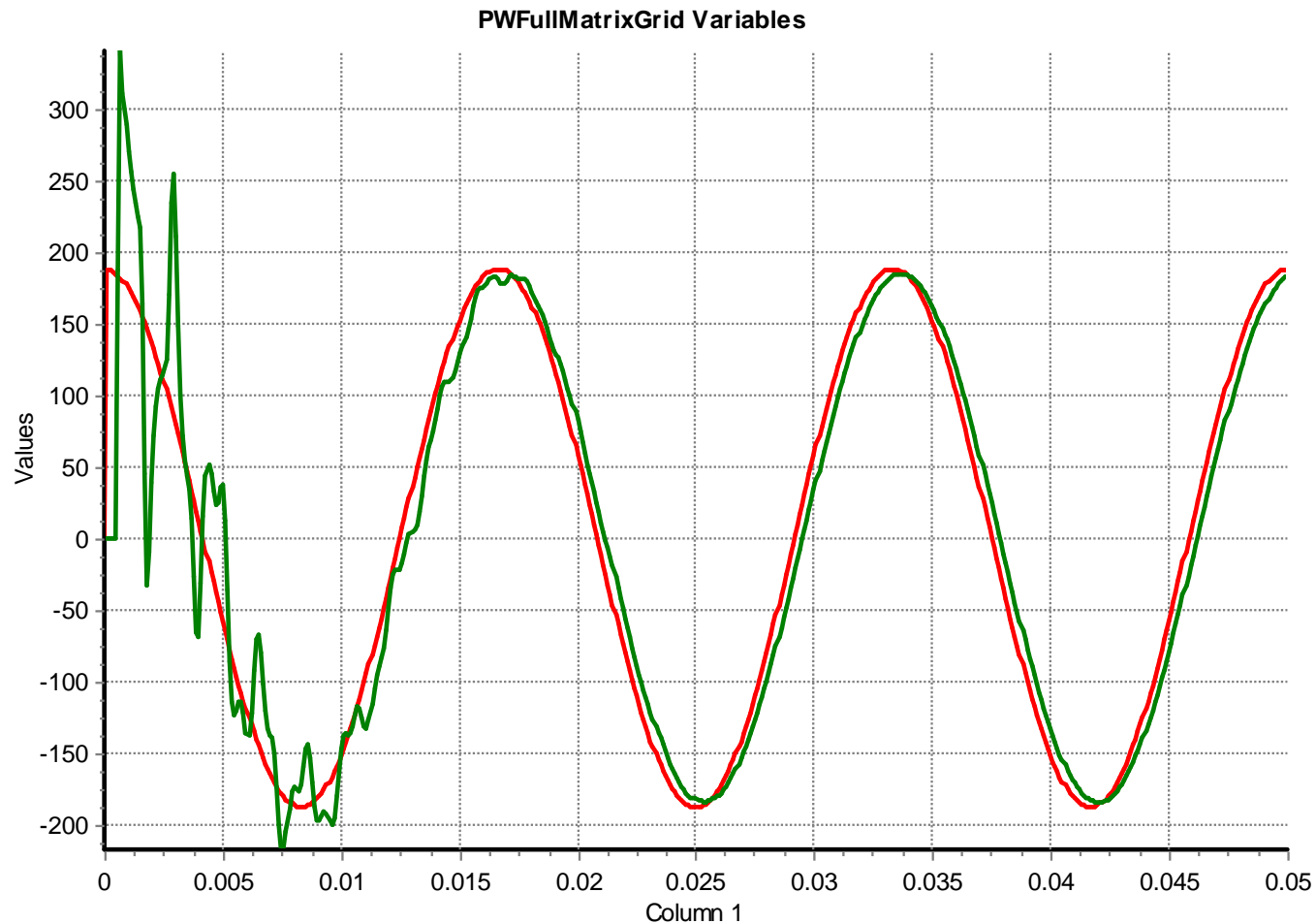

Red is the sending end voltage (in kv), while green is the receiving end voltage. Note the approximate voltage doubling at the receiving end.

Example 2.1: First Three Cycles

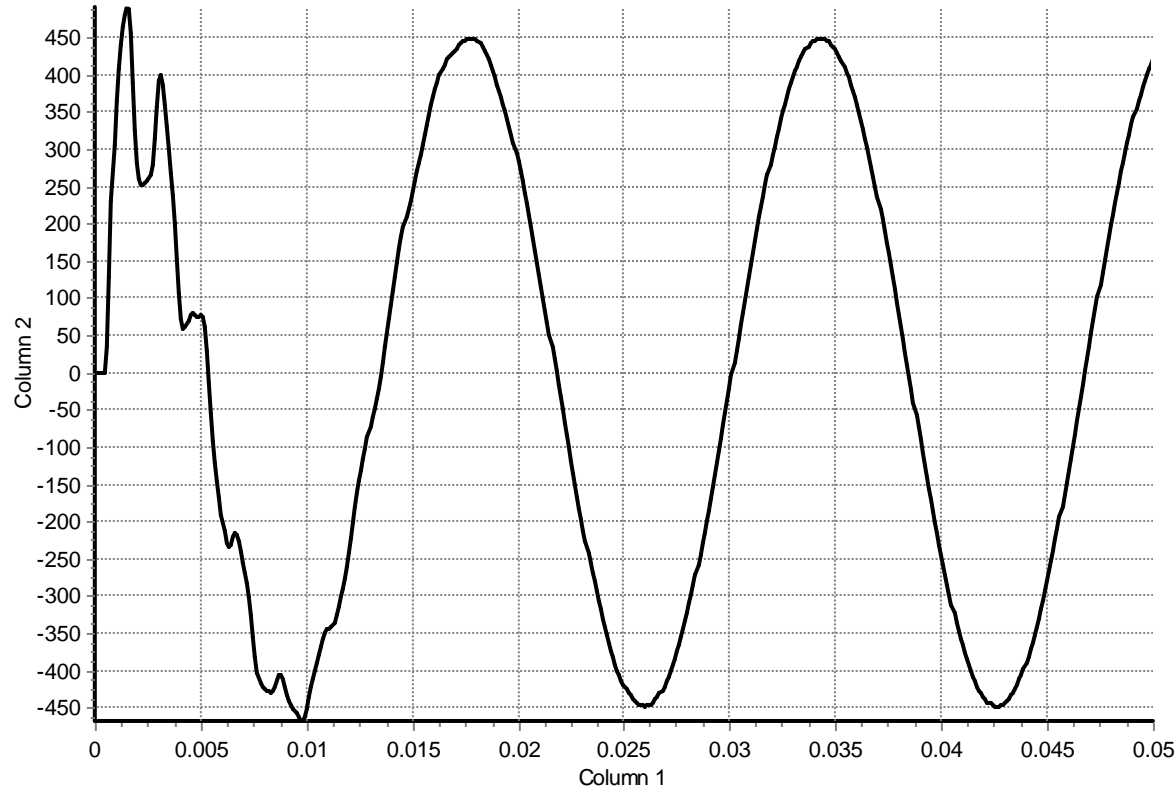

Graph shows the current (in amps) into the RL load over the first three cycles.

To get a **ballpark** value on the expected current, solve the simple circuit assuming the transmission line is just an inductor

$$I_{load,rms} = \frac{230,000 / \sqrt{3}}{400 + j94.2 + j56.5} = 311 \angle -20.6^\circ, \text{ hence a peak value of 439 amps}$$